


Online Test (ver A) - Boolean Logic & Number Systems

Name: Gurpreet Singh

Student #: 897163


Knowledge [9.5 / 10]

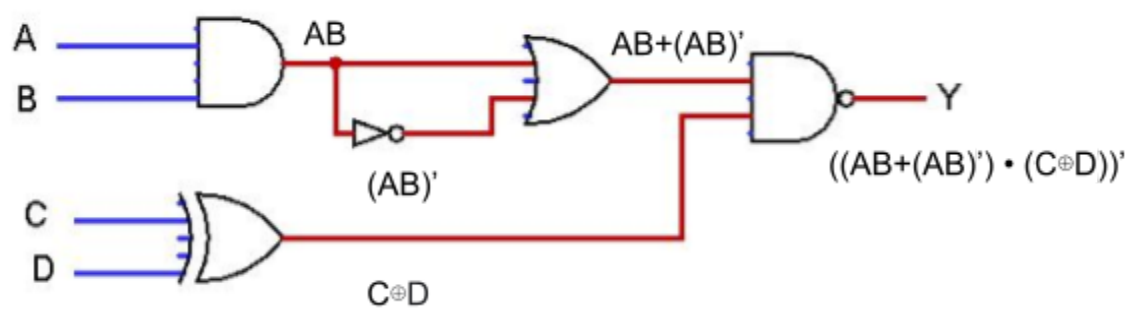1. Translate the following schematic into its boolean algebraic equivalent. Double-click on the image below and fill in each output at various stages of the circuit and then clearly write out the final answer. [3 marks] 3



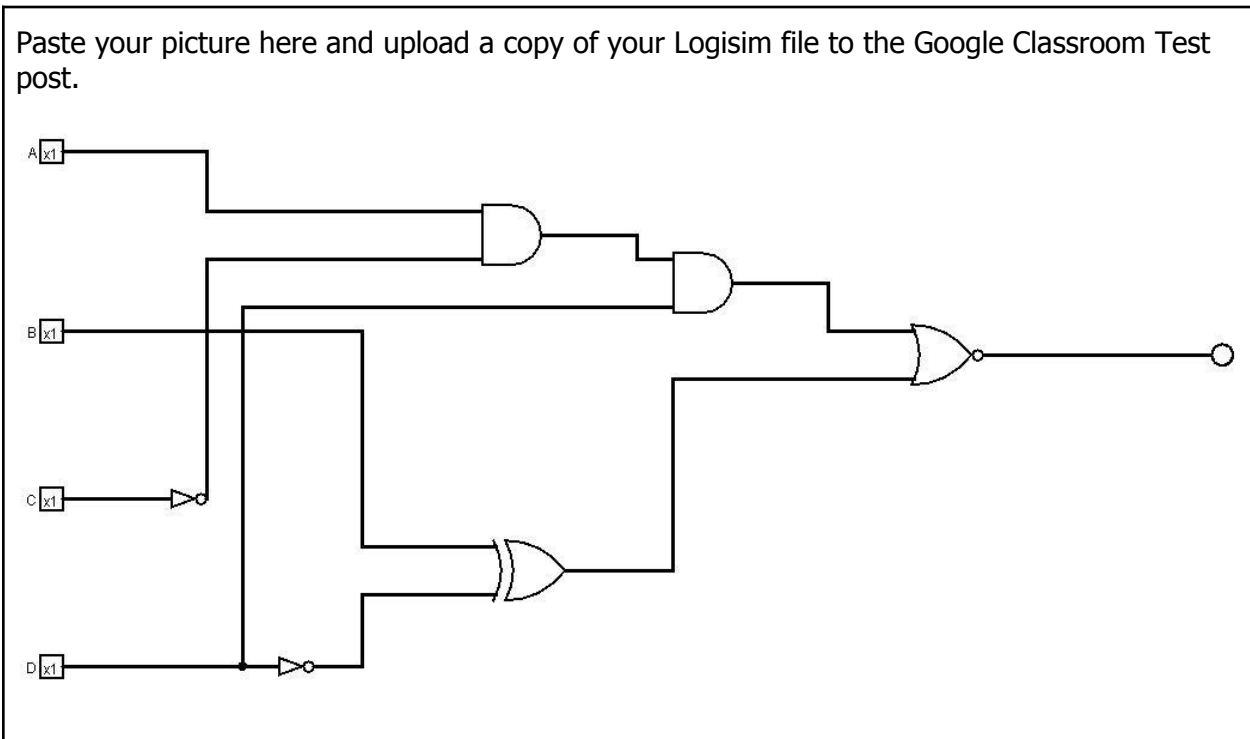2. Use the Logisim program to draw the schematic diagram for the boolean algebraic expression. Export it as a JPG and paste it in the box below. [4 marks] 4 Do not have more than two inputs per gate. Here is the equation:

$$A \overline{C} D + (B \oplus \overline{D})$$



Online Test (ver A) - Boolean Logic & Number Systems

3. Simplify the following expression using ONLY theorems and identities used in class. Do not use K-Maps. [3 marks] 2.5

$$\overline{AB} (\overline{A} + B) (\overline{B} + B)$$

Step #	Simplified Equation	Basic Simplification Rule or explanation
	$(AB)' (A' + B) (B' + B)$	$X' + X = 1$
1	$(AB)' (A' + B) (1)$	$A \cdot 1 = A$
2	$(AB)' (A' + B)$	DeMorgan's Theorem $\overline{(X \cdot Y)} = \overline{X} + \overline{Y}$
3	$(A'+B')(A'+B)$	Factor A'
4	$A'+B'B$ Missing steps in between. You need to expand the brackets	$X' \cdot X = 0$
5	$A' + 0$	$X + 0 = X$
6	A' Correct answer here	Final Solution