


D & JK FLIP FLOPS

(Sequential Circuits)

D Flip Flop


- ❖ Also Known as Data Flip flop
- ❖ Can be constructed from RS Flip Flop or JK Flip flop by addition of an inverter.
- ❖ Inverter is connected so that the R input is always the inverse of S (or J input is always complementary of K).
- ❖ The D flip flop will act as a storage element for a single binary digit (Bit).

D Flip flop symbol

 

D Flip Flop - Symbol

PGT

 

NGT


 


Figure 4.6.2 : D Flip flop symbol using JK Flip Flop / SR Flip Flop


JK Flip Flop - Symbol

- ❖ Another types of Flip flop is JK flip flop.
- ❖ It differs from the RS flip flops when $J=K=1$ condition is not indeterminate but it is defined to give a very useful changeover (toggle) action.
- ❖ Toggle means that Q and Q' will switch to their opposite states.
- ❖ The JK Flip flop has clock input C_p and two control inputs J and K .
- ❖ Operation of Jk Flip Flop is completely described by truth table in Figure 4.3.3.

❖ **PGT JK Flip flop symbol**

 

❖ **NGT JK Flip flop symbol**

 


JK Flip Flop – Truth Table And Logic Circuit

Truth Table for JK
Flip Flop


clock	J	K	Q	Q'	STATUS
↑	0	0	Q	Q'	HOLD (No Change)
↑	0	1	0	1	RESET
↑	1	0	1	0	SET
↑	1	1	Q'	Q	Toggle

JK FLIP FLOP LOGIC
CIRCUIT

 

JK Flip Flop - waveforms

 Example: Determine the output of PGT clocked JK flip flop for the given input waveforms which the Q initially 0.




JK Flip Flop - Completed Diagram

Example: Determine the output of PGT clocked JK flip flop for the given input waveforms which the Q initially 0.




JK Flip Flop - waveforms

 Exercise: Determine the output of
NGT clocked JK flip flop for the
given input waveforms which the
Q initially 0.



 Exercise: Determine the output of
PGT clocked JK flip flop for the
given input waveforms which the
Q initially 0.



JK Flip Flop with Asynchronous Input

- ❖ The J and K inputs are called synchronous inputs since they only influence the state of the flip flop when the clocked pulse is present.
- ❖ This flip flop can also have other inputs called Preset (or SET) and clear that can be used for setting the flip flop to 1 or resetting it to 0 by applying the appropriate signal to the Preset and Clear inputs.
- ❖ These inputs can change the state of the flip flop regardless of synchronous inputs or the clock.

JK Flip Flop with Preset and Clear

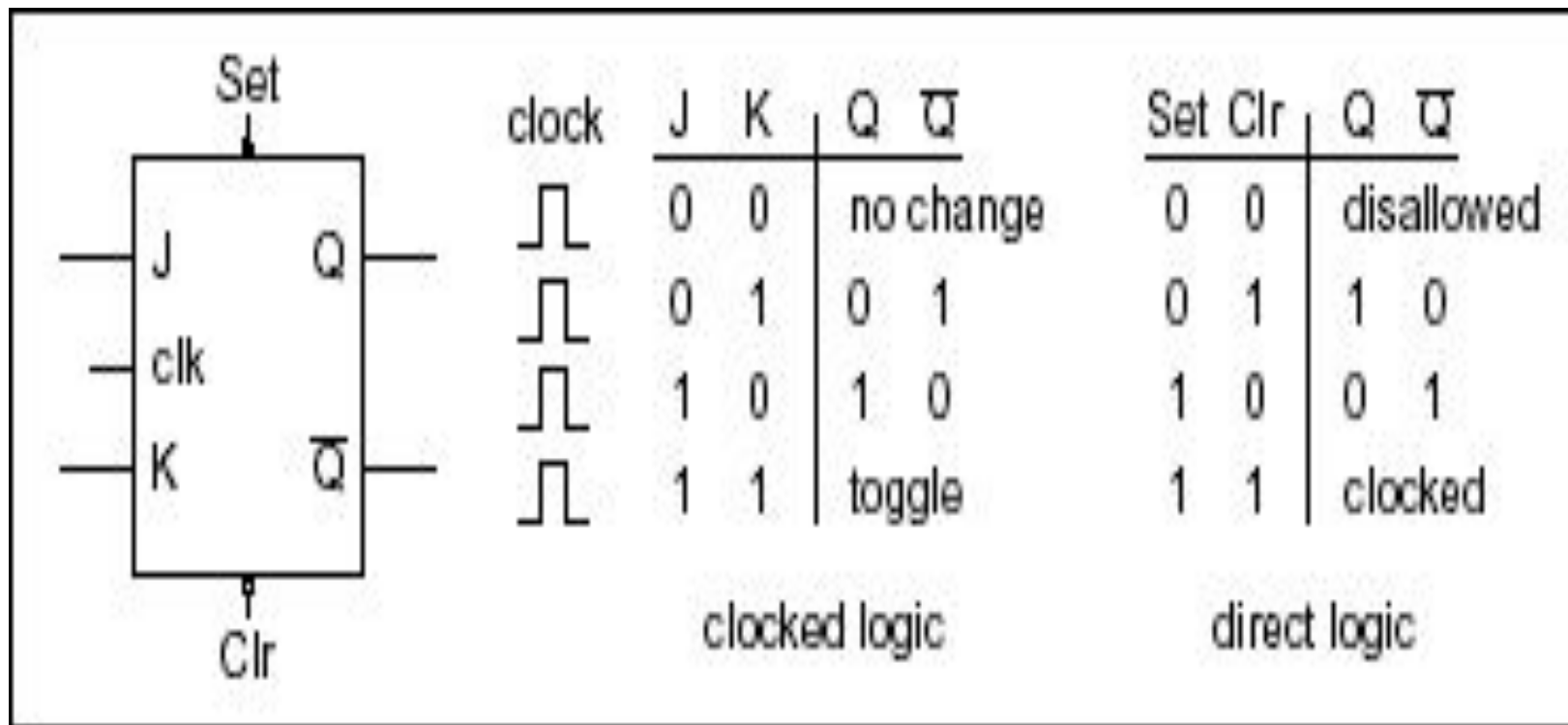


Figure 4.4.1 : Symbol and Truth Table

JK Flip Flop with Asynchronous Input

❖ **Example** : The output of clocked JK flip flop which output **initially 0** for the given input waveforms. Clock (NGT)

