
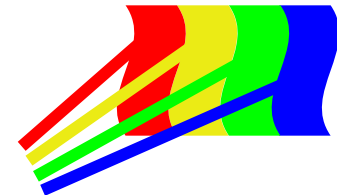


# Digital Electronics

## Principles & Applications

### Seventh Edition

#### Arithmetic Circuits

 

# INTRODUCTION

- **Binary Addition**
- **Half Adders**
- **Full Adders**
- **Parallel Adding**

# Binary Addition

- Conceptually similar to decimal addition
- *Example:* Add the binary numbers 1010 and 11


A diagram illustrating the binary addition of 1010 and 11. The numbers are aligned vertically, with 1010 on top and 11 below it. A horizontal line separates the addends from the result. The result, 1101, is written below the line. A red curved arrow labeled '(carry) 1' points from the sum of the second column (0 + 1 = 1) to the third column, indicating a carry of 1.

$$\begin{array}{r} \text{(carry)} \\ 1 \\ 1010 \\ + \quad 11 \\ \hline 1101 \end{array}$$


# Half Adder

- Logic device that adds two binary numbers
- Only adds Least Significant Digit (LSD) column (1s column) in binary addition

Logic  
Symbol:

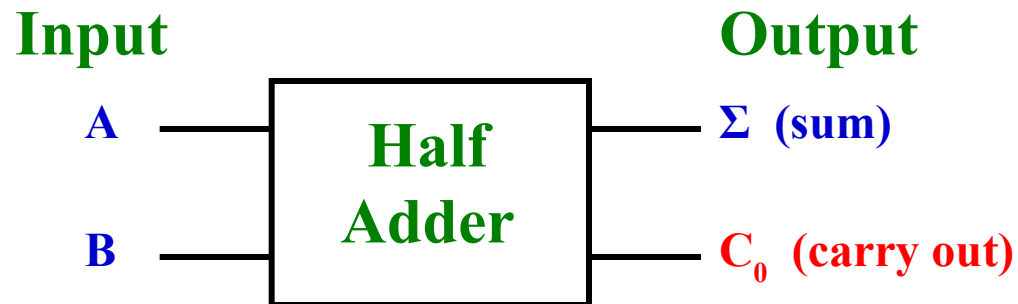


Logic  
Diagram:

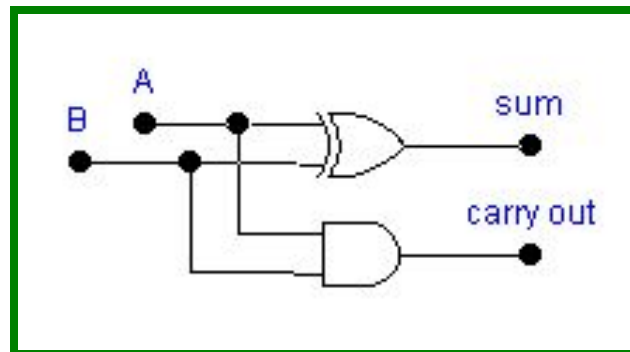

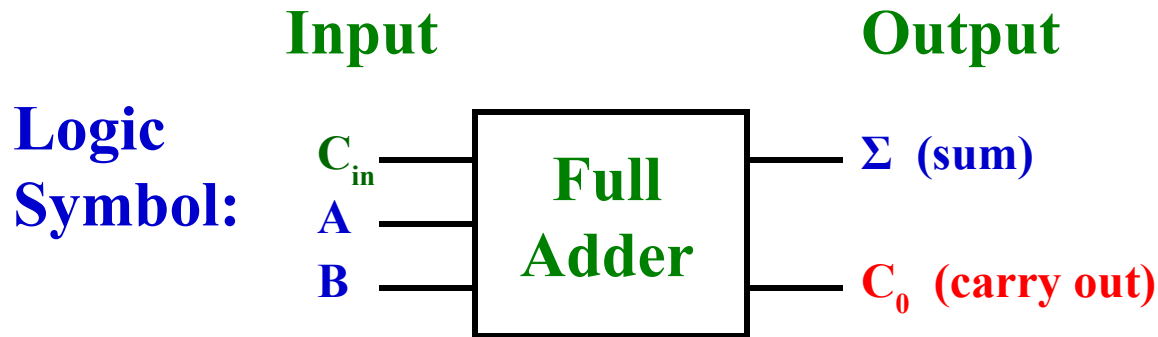
# Full Adder

Used for adding binary place values other than the 1s place




Logic Diagram:

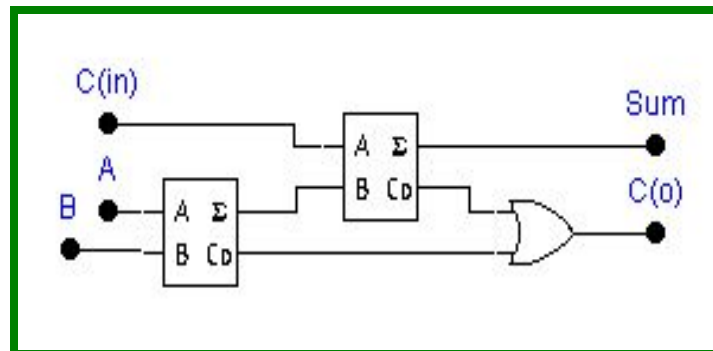
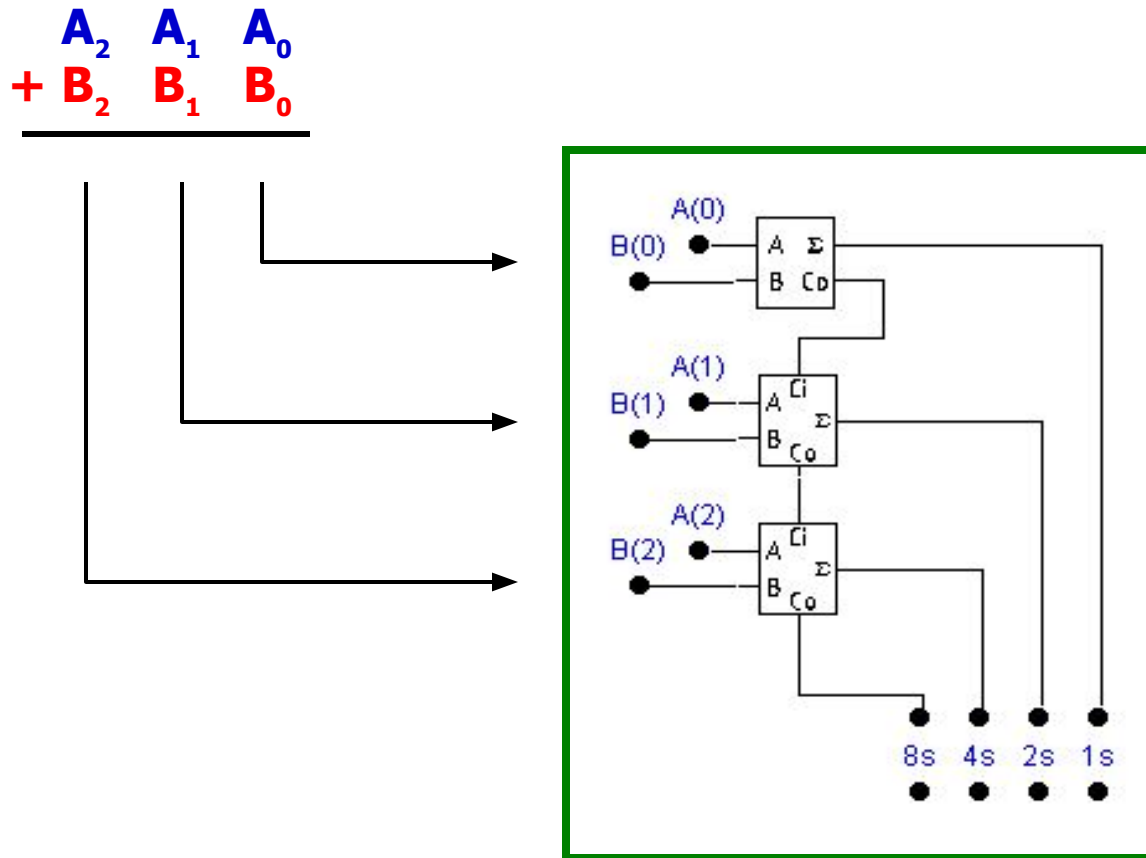
# Parallel Adding


- Use half adder for LSD
- Use full adder for other digits



# Parallel Adder

Enter binary numbers  
to be added

1 1 1 0 + 0 1 1 0

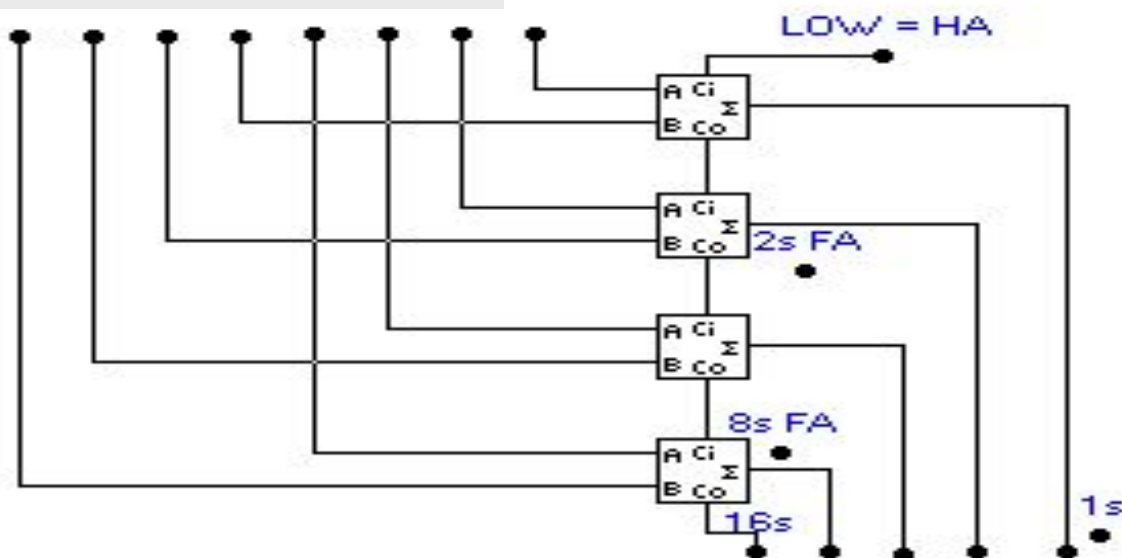

1 0 1 0 0

SUM appears here


Parallel adders are available in IC form.

1s place uses half-adder

2s, 4s, 8s places use full adders
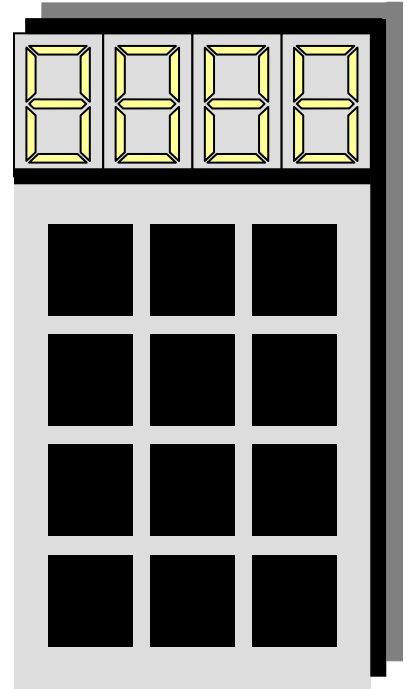
# Practical Suggestion for Binary Math

- **Use a scientific calculator.**
- **Most scientific calculators have DEC, BIN, OCT, and HEX modes and can either convert between codes or perform arithmetic in different number systems.**
- **Most scientific calculators also have other functions that are valuable in digital electronics such as AND, OR, NOT, XOR, and XNOR logic functions.**





# REVIEW

- **Binary Addition**
- **Half Adders**
- **Full Adders**
- **Parallel Adding**