


Student Name:

Gurpreet Singh


TEJ4M0 Electronics Review

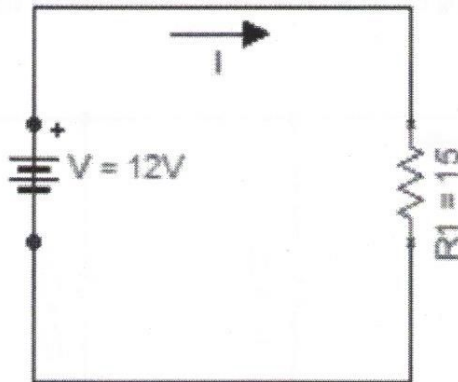1. According to Kirchhoff's Current Law, the total current entering a junction must equal the total current **leaving** the junction.
2. Kirchhoff's Voltage Law is used in **parallel** circuits.
3. Kirchhoff's Current Law is used in **parallel** circuits.
4. Since series circuits contain only one current path, therefore the current is the **same** everywhere.
5. Since parallel circuits contain more than one current path, therefore the total current is the sum of the individual currents.
6. Transistors are used to **amplify** weak signals and also as **switches** to disconnect other components.
7. Transistors have three connection points. These include the **collector**, **base**, and the **emitter**.
8. A 12 volt battery supplies power to a soldering iron with a resistance of 15 ohms. Using Ohm's Law, calculate how much current is being drawn by the soldering iron? Show your calculations.


$$\begin{aligned} I &= \frac{V}{R} \\ &= \frac{12}{15} \\ &= 0.8 \text{ A} \end{aligned}$$



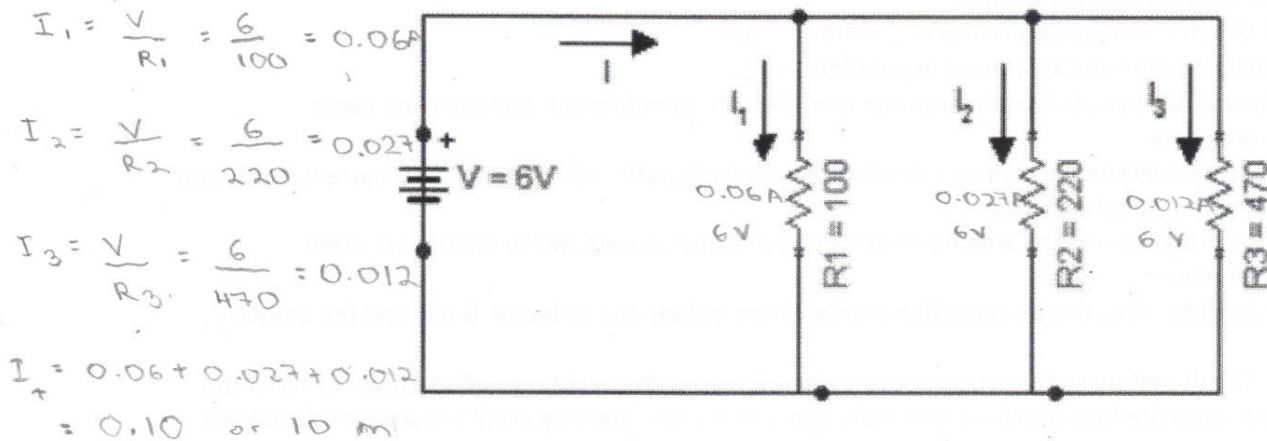9. Using Ohm's Law and Kirchoff's voltage law, calculate the current flowing through each resistor and the total current flowing through the circuit below ($R_1 = 100\Omega$, $R_2 = 220\Omega$, $R_3 = 470\Omega$). Show your calculations. All current values should be provided in milliamps.



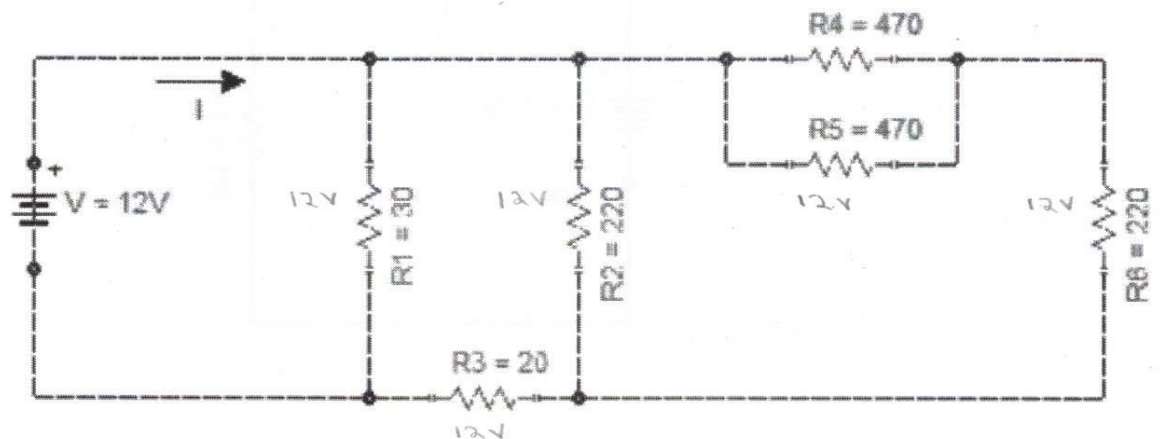
10. Simplify the following circuit and determine the value for total circuit current (I). Show calculations.



11. For the circuit below, calculate all of the values below. Show all calculations.

$R_T = 50\Omega$	$I_T = 2.31A$	$P_T = 231W$
$I_{R1} = 0.3125A$	$V_{R1} = 31.25V$	$P_{R1} = 9.76W$
$I_{R2} = 0.3125A$	$V_{R2} = 68.75V$	$P_{R2} = 21.48W$
$I_{R3} = 1A$	$V_{R3} = 100V$	$P_{R3} = 100W$
$I_{R4} = 0.66A$	$V_{R4} = 100V$	$P_{R4} = 66W$
$I_{R5} = 0.33A$	$V_{R5} = 100V$	$P_{R5} = 33W$

Student Name: _____

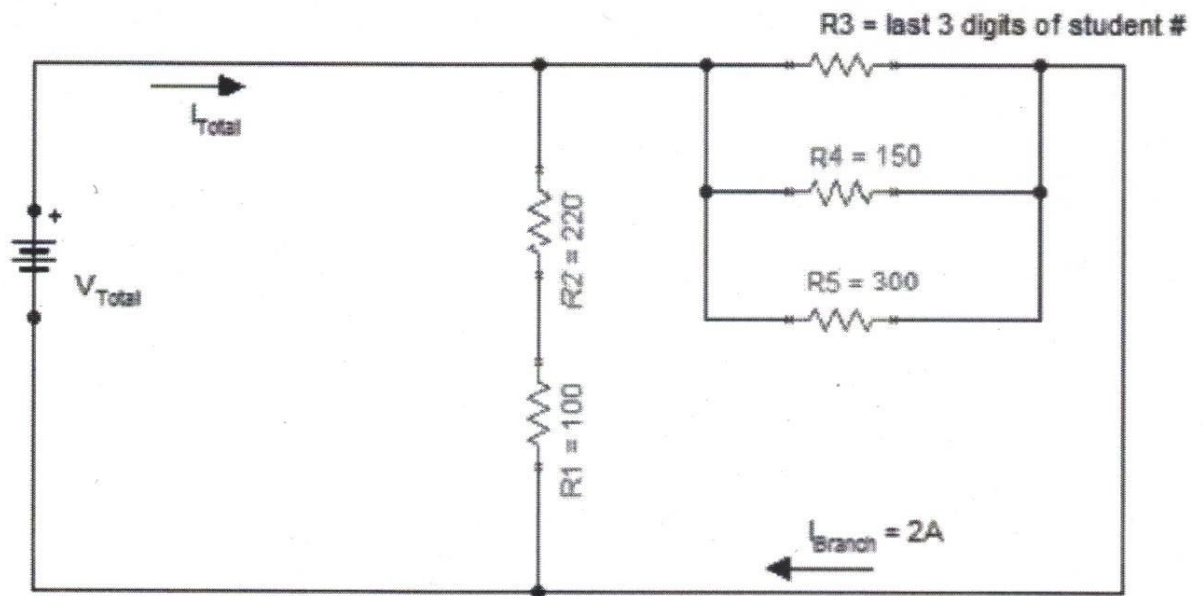

Summary

$$V_1 = I_1 R_{1,2}$$

$$= (0.3125)(100)$$

$$= 31.25$$

$$V_3 = 100 \text{ V}$$

$$V_4 = 100 \text{ V}$$

$$V_2 = I_2 R_{1,2}$$

$$= (220)(0.3125)$$

$$= 68.75 \text{ V}$$

$$V_5 = 100 \text{ V}$$

$$I_1 = \frac{V_1}{R_1}$$

$$= \frac{31.25}{100}$$

$$= 0.3125$$

$$I_2 = \frac{V_2}{R_2}$$

$$= \frac{68.75}{220}$$

$$= 0.3125 \text{ A}$$

$$I_3 = \frac{V_3}{R_3}$$

$$= \frac{100}{100}$$

$$= 1 \text{ A}$$

$$I_4 = \frac{V_4}{R_4}$$

$$= \frac{100}{150}$$

$$= 0.66 \text{ A}$$

$$I_5 = \frac{V_5}{R_5}$$

$$= \frac{100}{300}$$

$$= 0.33 \text{ A}$$

$$P_1 = V_1 I_1$$

$$= (31.25)(0.3125)$$

$$= 9.76 \text{ W}$$

$$P_2 = V_2 I_2$$

$$= (68.75)(0.3125)$$

$$= 21.48 \text{ W}$$

$$P_3 = V_3 I_3$$

$$= (100)(1)$$

$$= 100 \text{ W}$$

$$P_4 = V_4 I_4$$

$$= (100)(0.66)$$

$$= 66 \text{ W}$$

$$P_5 = V_5 I_5$$

$$= (100)(0.33)$$

$$= 33 \text{ W}$$

TEJ 4 MO Electronics Review


$$9) I_1 = \frac{V}{R_1} = \frac{6}{100} = 0.06A$$

$$I_2 = \frac{V}{R_2} = \frac{6}{220} = 0.027A$$


$$I_3 = \frac{V}{R_3} = \frac{6}{470} = 0.012A$$

$$I_T = 0.06 + 0.027 + 0.012 = 100 \text{ mA}$$


10)

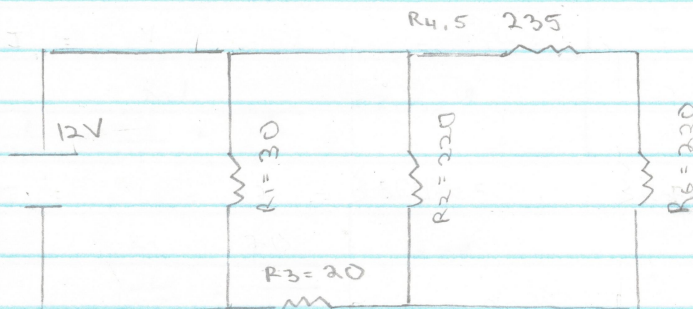

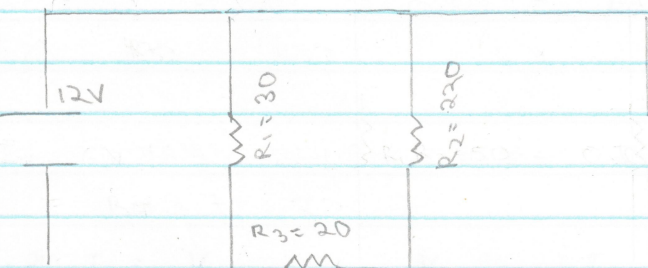
$$R_{4,5} = (470)(470) / (470 + 470) = 235 \Omega$$




$$R_{4,5,6} = 235 + 220 = 455 \Omega$$

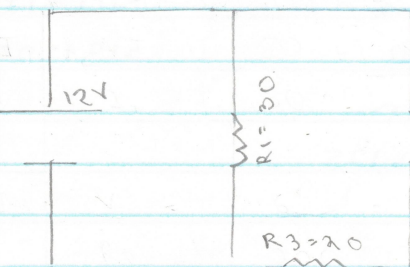
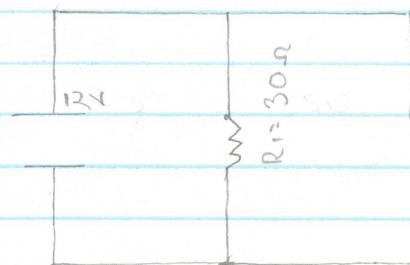
$$R_{2,4,5,6} = (455)(220) / (455 + 220) = 148.29 \Omega$$



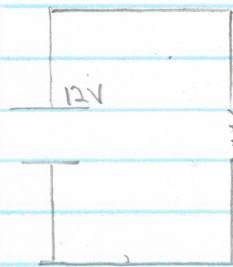
$$R_{2,3,4,5,6} = 148.29 + 20 = 168.29 \Omega$$



$$R_{1,2,3,4,5,6} = \frac{(168.29)(30)}{168.29 + 30} = 25.46$$


$$I_T = \frac{V_T}{R_T} = \frac{12V}{25.46} = 0.47 \text{ or } 470 \text{ mA}$$

11)

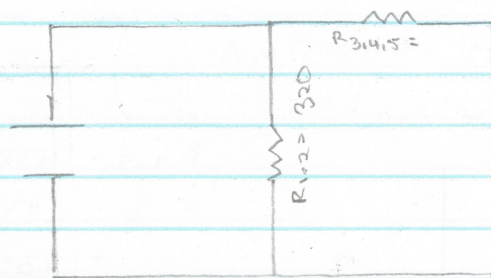

$$R_{1,2} = 220 + 100 = 320 \Omega$$
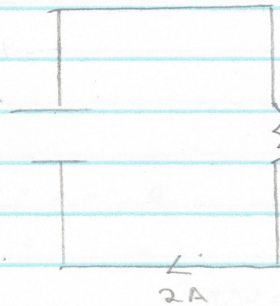
$$R_{3,4,5} = \frac{1}{\frac{1}{100} + \frac{1}{150} + \frac{1}{300}} = 50$$



$$R_T = \frac{1}{\frac{1}{320} + \frac{1}{50}} = 43.24$$

$$V_T = (2) \cdot (R_{1,2,3}) = (2)(50) = 100V$$

$$I_{1,2} = \frac{V}{R_{1,2}} = \frac{100}{320} = 0.3125$$

$$V_1 = I_1 \cdot R_{1,2} = (0.3125)(100) = 31.25V$$

$$V_2 = I_2 \cdot R_{1,2} = (220)(0.3125) = 68.75V$$

$$I_3 = 100, I_4 = 100, I_5 = 100$$