

Table <-> Expression Worksheet

Convert from a truth table to an algebraic expression

Input	Output	Expression:
ABC	Y	$\overline{A}\overline{B}\overline{C} + ABC$
0 0 0	0	
0 0 1	0	
0 1 0	1	
0 1 1	0	
1 0 0	0	
1 0 1	0	
1 1 0	0	
1 1 1	1	

Input	Output	Expression:
ABC	Y	$\overline{ABC} + ABC$
0 0 0	1	
0 0 1	0	
0 1 0	0	
0 1 1	0	
1 0 0	0	
1 0 1	0	
1 1 0	0	
1 1 1	1	

Convert from a minterm expression to a truth table

$\overline{A}\cdot\overline{B}\cdot\overline{C} + \overline{A}\cdot B\cdot C + A\cdot B\cdot\overline{C} = Y$

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

Table <-> Expression Worksheet

$\bar{A} \cdot \bar{B} + A \cdot B \cdot C = Y$

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Worksheet

1. Convert the truth table below into an equivalent algebraic expression. **Inputs:** A, B **Output:** Y

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Minterm Expression: $\bar{A}B + A\bar{B}$

Is there a way we can simplify this further? **No** If so, how?

Write down your newly learned theorem:

Input	Output
ABC	Y
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0

Minterm Expression:
 $\bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C}$

Table <-> Expression Worksheet

1	0	1	1
1	1	0	0
1	1	1	1

Can your expression be simplified? If so, show all of your steps below.

This expression can be simplified.

By using

$$\overline{A}\overline{B}\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + ABC$$

$$\overline{A}B(1\overline{C} + 1C) + A\overline{B}\overline{C} + ABC$$

$$\overline{A}B(\overline{C} + C) + AC(\overline{B} + B)$$

$$\overline{A}B(1) + AC(1)$$

$$\overline{A}B + AC$$

Next, draw the simplified version of your circuit below.

