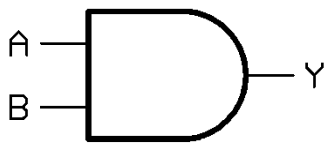

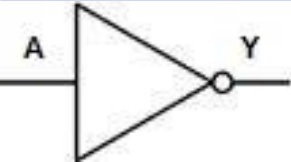
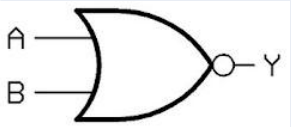
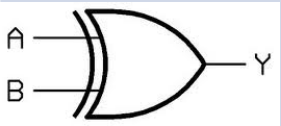
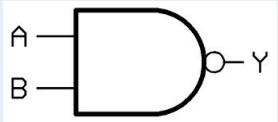


Digital Logic Gates – ***Truth Tables to Expressions***


Table of Gate Representations

Schematic	Gate	Algebraic Symbol	Boolean Equation
	AND	•	$Y=A \bullet B$
	OR	+	$Y=A+B$
	NOT	–	$Y=\bar{A}$
	NOR	– +	$Y=\overline{A+B}$
	XOR	\oplus	$Y=A \oplus B$
	NAND	– •	$Y=\overline{A \bullet B}$


“Tools of the Trade” for Solving Logic Problems

- Gate symbols
- Truth tables
- Boolean expressions

Combinational logic circuits:

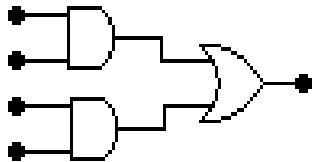

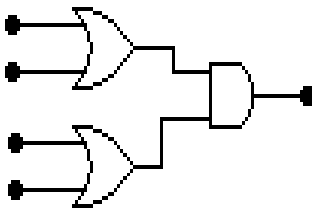AND-OR pattern of gates
from
Sum-of-products Boolean expression such as:
 $AB + CD = Y$
(Also called a min-term Boolean expression)



OR-AND pattern of gates
from
Product-of-sums Boolean expression such as:
 $(A+B)(C+D) = Y$
(Also called a max-term Boolean expression)

Boolean Expression from Truth Table

Write the Boolean expression that describes the logic in this truth table.

Truth Table

Input Output

ABC Y

0 0 0 0

0 0 1 0

0 1 0 1

0 1 1 0

1 0 0 0

1 0 1 0

1 1 0 0

1 1 1 1

Step 1: Focus only on the truth table lines with outputs of 1.

Step 2: AND the inputs for these two lines and logically OR the ANDed groups.

$$\bar{A} \cdot B \cdot \bar{C} + A \cdot B \cdot C = Y$$

Minterm Boolean expression: $\bar{A} B \bar{C} + A B C = Y$



QUIZ

Truth Table

Input ABC	Output Y
0 0 0	1
0 0 1	0
0 1 0	0
0 1 1	0
1 0 0	0
1 0 1	0
1 1 0	0
1 1 1	1

Write the Boolean expression that describes the logic in this truth table.

$$\bar{A} \cdot \bar{B} \cdot \bar{C} + A \cdot B \cdot C = Y$$

Minterm Boolean expression: $\bar{A} \bar{B} \bar{C} + A B C = Y$

Truth Table From Boolean Expressions

Fill in a truth table from a minterm Boolean Expression.

Minterm Boolean expression: $\bar{A} \cdot \bar{B} \cdot \bar{C} + \bar{A} \cdot B \cdot C + A \cdot B \cdot \bar{C} = Y$

Step 1: Place three 1s in output column.

Step 2: Place five 0s in blanks in output column of truth table.

Truth Table

Input ABC	Output Y
--------------	-------------

0 0 0	1
0 0 1	0
0 1 0	0
0 1 1	1
1 0 0	0
1 0 1	0
1 1 0	1
1 1 1	0

Truth Table from Boolean Expressions

Fill in a truth table from a minterm Boolean Expression.

Minterm Boolean expression: $\bar{A} \cdot \bar{B} + A \cdot B \cdot C = Y$

Truth Table

Input Output
ABC Y

0 0 0 1

0 0 1 1

0 1 0 0

0 1 1 0

1 0 0 0

1 0 1 0

1 1 0 0

1 1 1 1

Step 1: Place single 1 output column for term with three variables.

Step 2: Place two 1s in output column for term with two variables.

Step 3: Fill in 0s.