
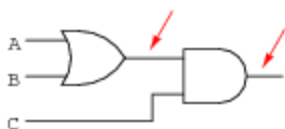


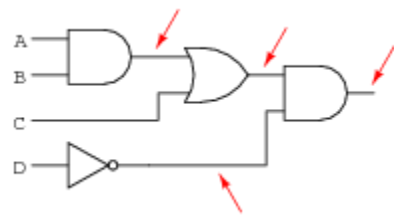
11. Convert the following logic gate circuit into a Boolean equation, writing Boolean sub-expressions next to each gate output in the diagram:



12. Convert the following logic gate circuit into a Boolean equation, writing Boolean sub-expressions next to each gate output in the diagram:



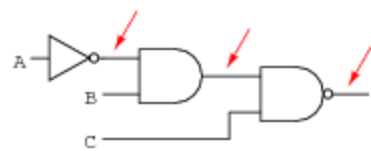13. Convert the following logic gate circuit into a Boolean equation, writing Boolean sub-expressions next to each gate output in the diagram:



14. Draw the following logic gate circuit based on the expressions below:

$(AB + C)D$

$(A + B)(B + C)$

$A'B + (B+C)'$  \*Note: A' means NOT A)  
\*(B+C)' means the NOT is applied to the result of B+C

# Logic Gate Worksheet

- |          |          |          |          |
|----------|----------|----------|----------|
| ✓ 1) OFF | ✓ 4) ON  | ✓ 7) ON  | ✓ 10) ON |
| ✓ 2) ON  | ✓ 5) OFF | ✓ 8) OFF |          |
| ✓ 3) OFF | ✓ 6) ON  | ✓ 9) OFF |          |

