

# Electronics Review



# What's Included...

- What's an Electrical Circuit?
- Electrical Quantities (V, I, R)
- Basic Components
  - Resistors, Batteries, Diodes, Light Emitting Diodes (LEDs), Transistors, Capacitors
- Ohm's & Kirchhoff's Laws
- Simple Circuits
- Series/Parallel Circuits


# What's an Electrical Circuit?

- At a minimum, what are the three parts of an electrical circuit?

# What's an Electrical Circuit?

- At a minimum, what are the three parts of an electrical circuit?

- Power Source
- Load
- Conductor

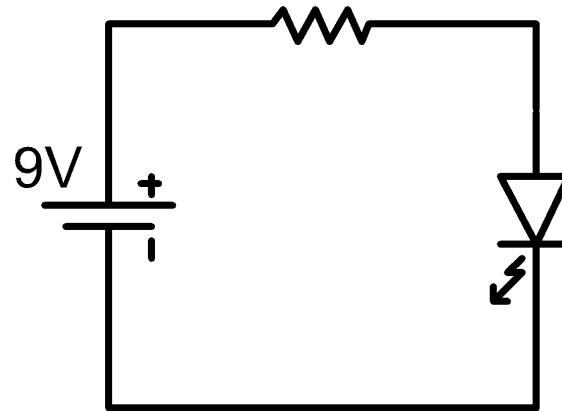

- Optionally, a circuit may include a “control device” such as a switch



# Three Main Invisible Quantities

- Voltage, symbol -  $V$ , units - Volts
  - Provides the “push”
- Current, symbol -  $I$ , units - Amperes (Amps)
  - Flow of Electrons
  - Amount of Current is dependent on Voltage and Resistance
- Resistance, symbol -  $R$ , units - Ohms ( $\Omega$ )
  - Limits the amount of current
  - Represents the “load” of the circuit



# Voltage Can Be Provided From...

- A battery:



- Computer Parallel port:

- Power Supply:

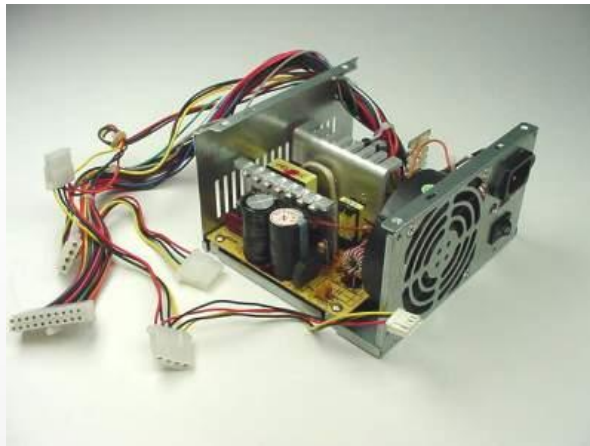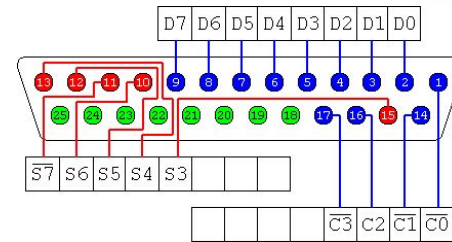

- Red: 5V
- Yellow: 12V
- Black: Ground


# Current

....is simply the flow of electrons


Q: Which way does current flow?

A: Depends upon convention!

*Electron Current Flow (-) to (+)*

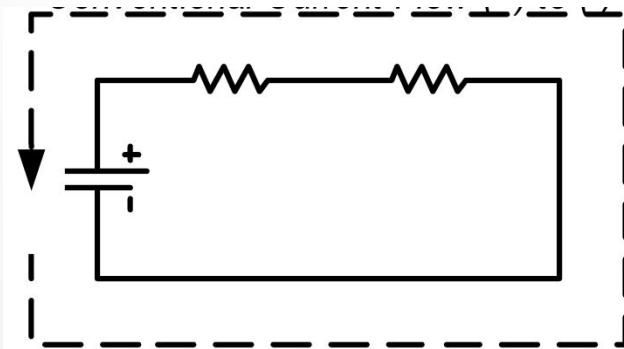

*Conventional Current Flow (+) to (-)*

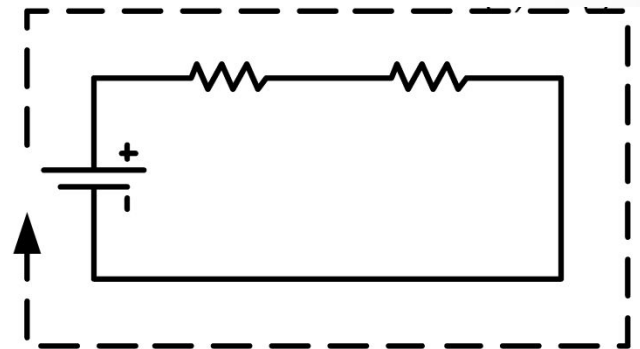

# Resistors – Basic Specs


- Can be rated by...
  - Resistance (Ohms,  $\Omega$ )
  - Tolerance (% of nominal value)
  - Power Rating (Watts)
- Schematic Symbol...







# Resistors – Types

- Fixed

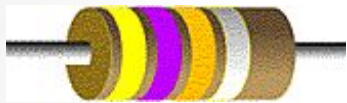


- Variable (Potentiometer, Rheostat)

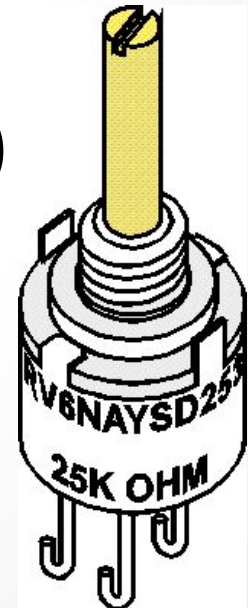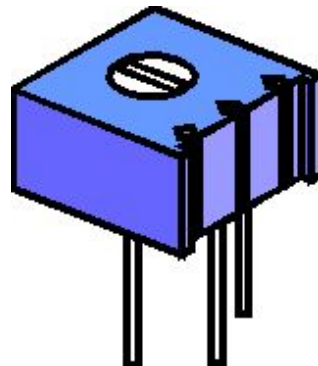


# Variable Resistors

## Potentiometer

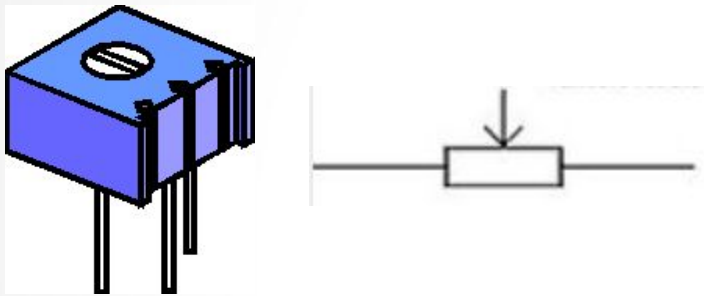

- Potentiometer is a three terminal variable resistor
- Used to vary voltage
- Applications include TV/sound volume control, voltage divider circuits etc.


## Rheostat

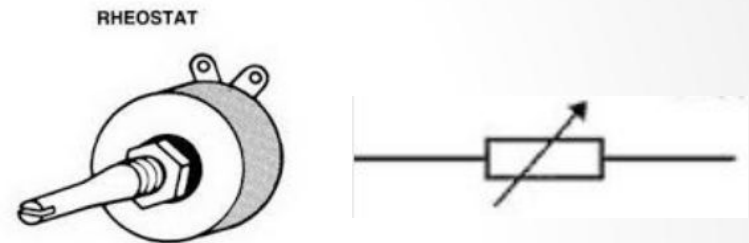

- Rheostat is a two terminal variable resistor
- Used to vary current
- Applications include motor speed control and other high current applications.


# Resistors – Colour Code

**Example: 4K7 or 4700 ohms (Carbon)**

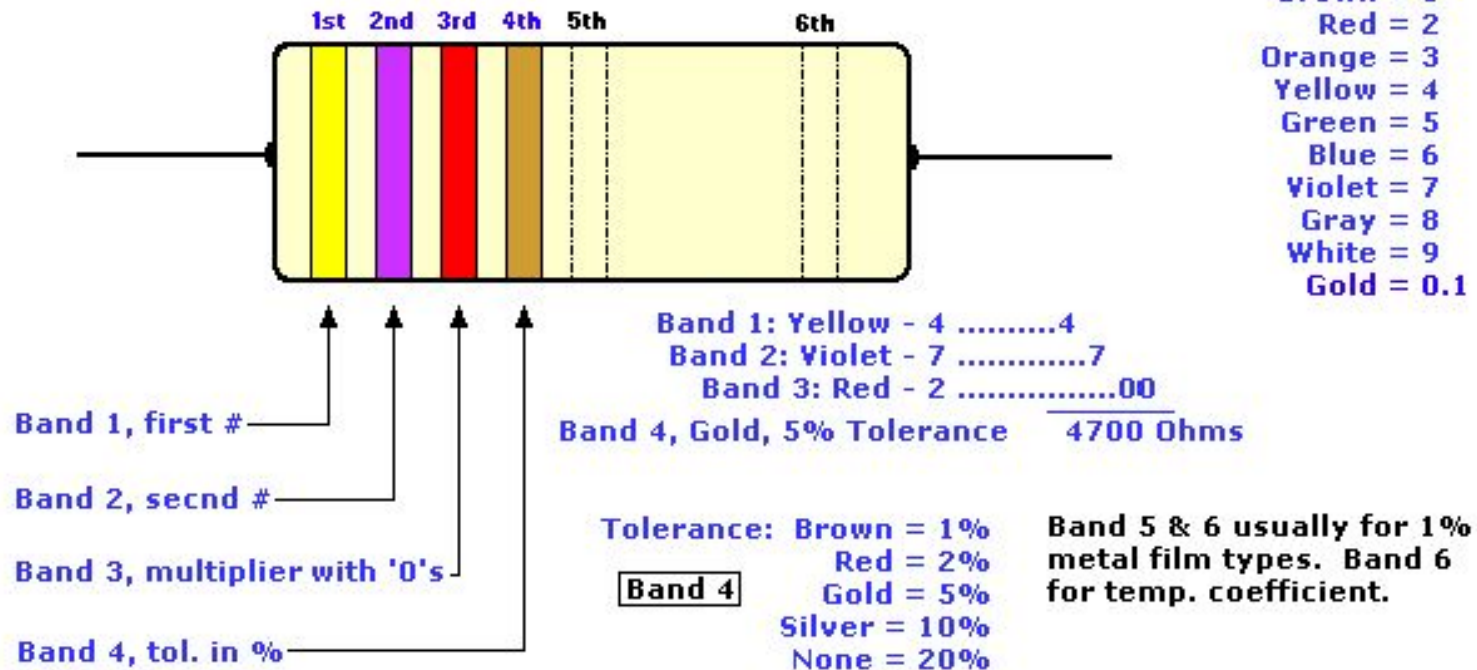

Reproduced by permission of Tony van Roon, 2002 <http://www.uoguelph.ca/~antoon>

# Resistors – Colour Code Example

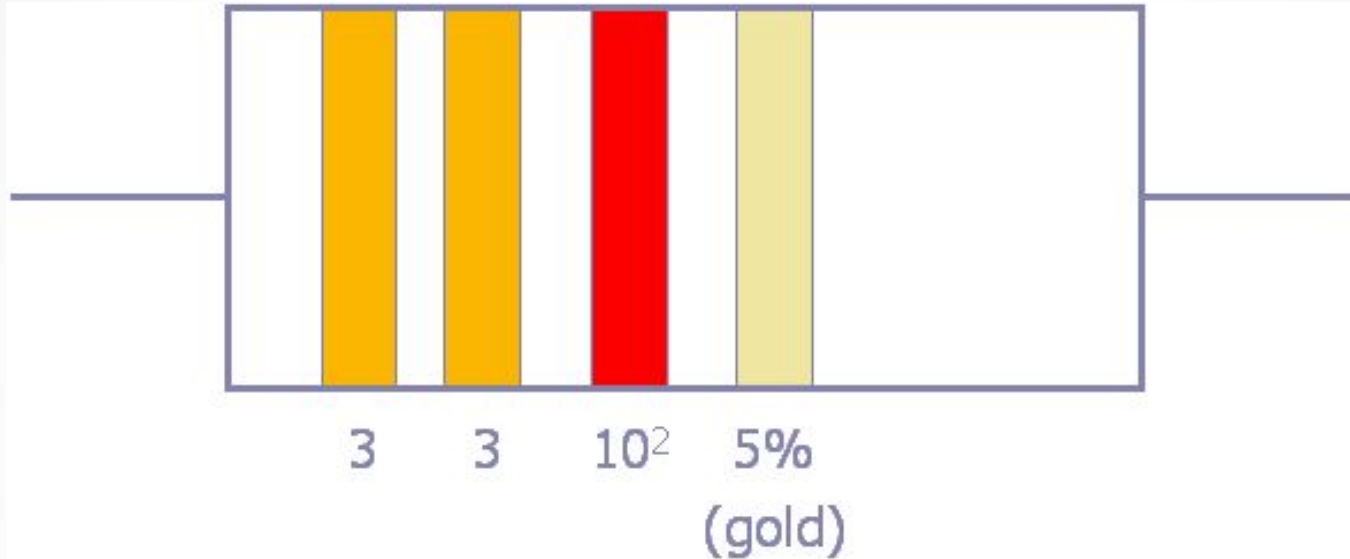

- 1<sup>st</sup> band: orange = 3
- 2<sup>nd</sup> band: orange = 3
- 3<sup>rd</sup> band: red = 2 (i.e. 10<sup>2</sup>)
- 4<sup>th</sup> band: gold = 5%

$$\begin{aligned} 33 \times 10^2 \\ &= 3300 \, \Omega \\ &= 3.3 \, \text{k}\Omega \end{aligned}$$

# Ohm's Law

“Current (I) is proportional to Voltage (V) and inversely proportional to Resistance (R)”


$$I = \frac{V}{R}$$

$$V = I \times R$$

$$R = \frac{V}{I}$$


$$P = I \times V$$

# Ohm's Law and Power Formulas

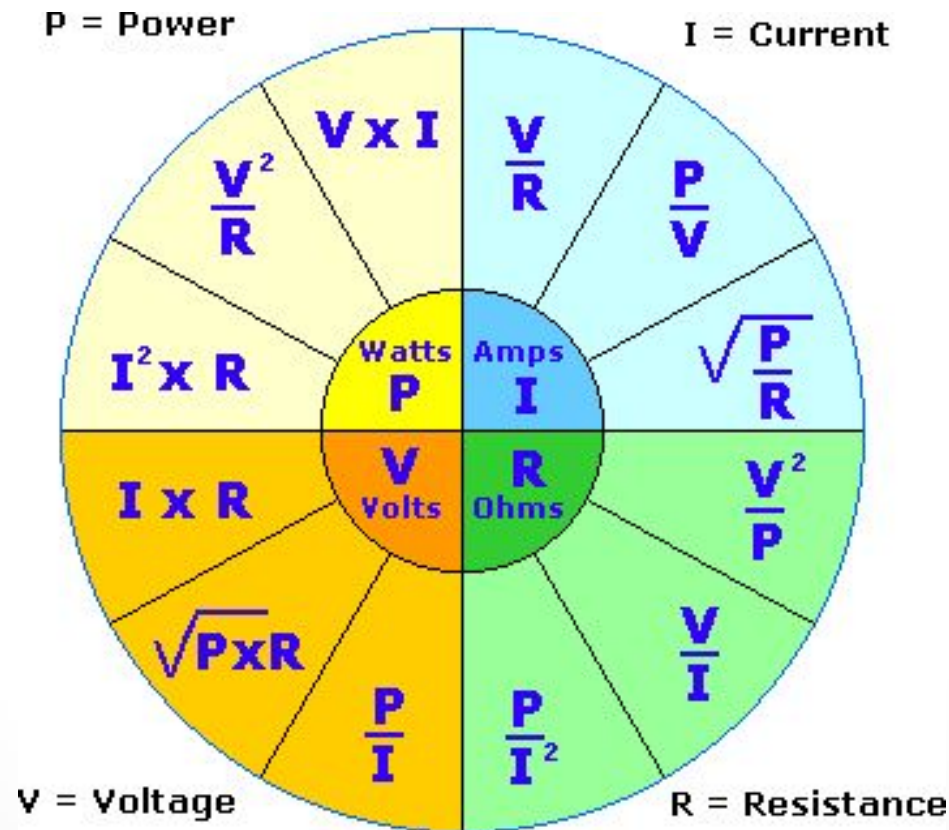

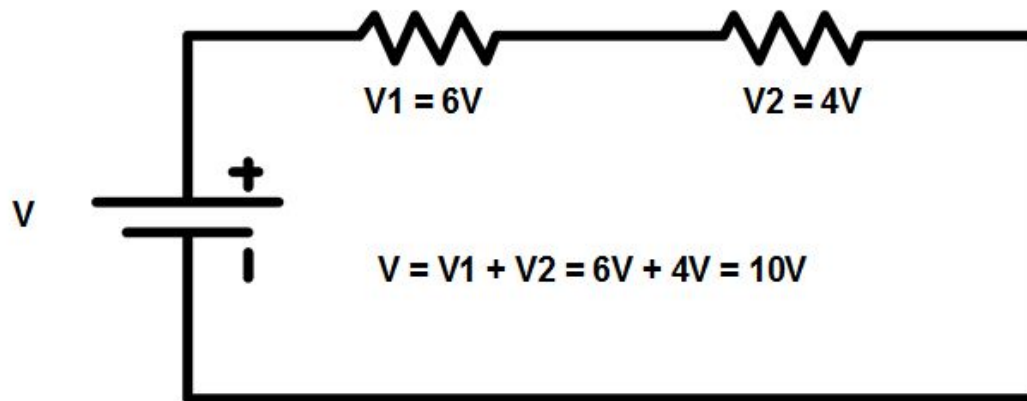
# Kirchhoff's Voltage Law

- Used in series circuits
- “The sum of the voltage drops equals the applied voltage”, or...
- “The sum of the voltage drops around a closed loop equals zero”


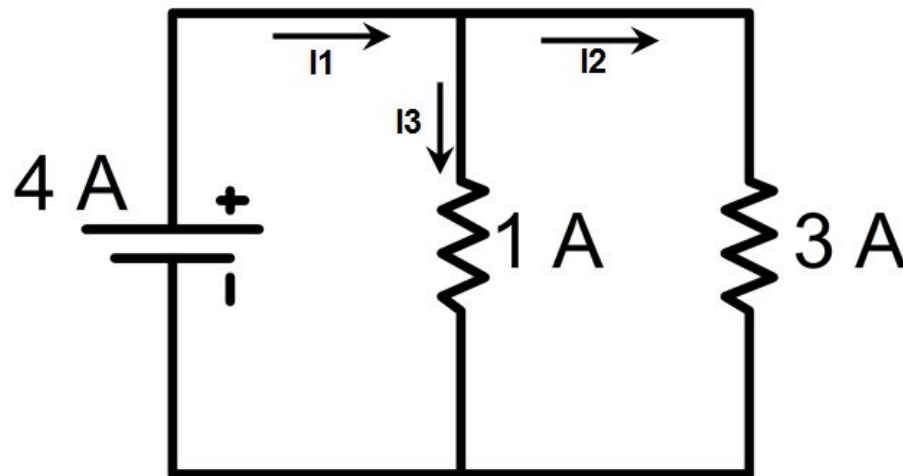
# Kirchhoff's Current Law

- “The total current entering a junction must equal the total current leaving the junction”
- Use in parallel circuits.




$$I_1 = I_2 + I_3 = 3A + 1A = 4A$$


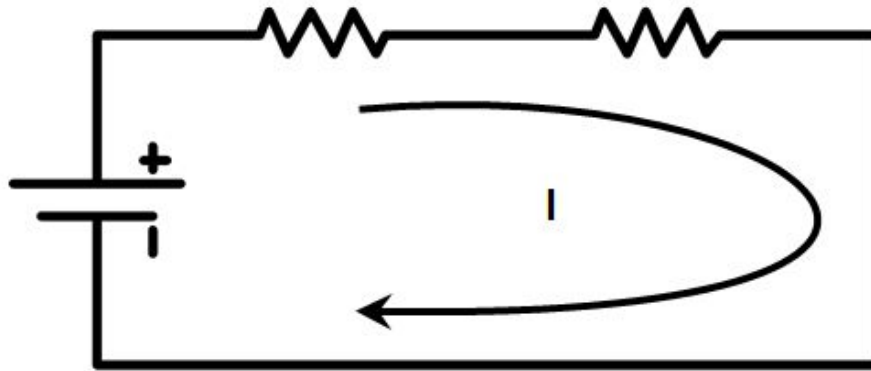
# Series Circuits

- One current path, therefore the current is the same everywhere




- Total resistance is the sum of the individual resistances

$$R_T = R_1 + R_2 + \dots$$

# Parallel Circuits

- More than one current path

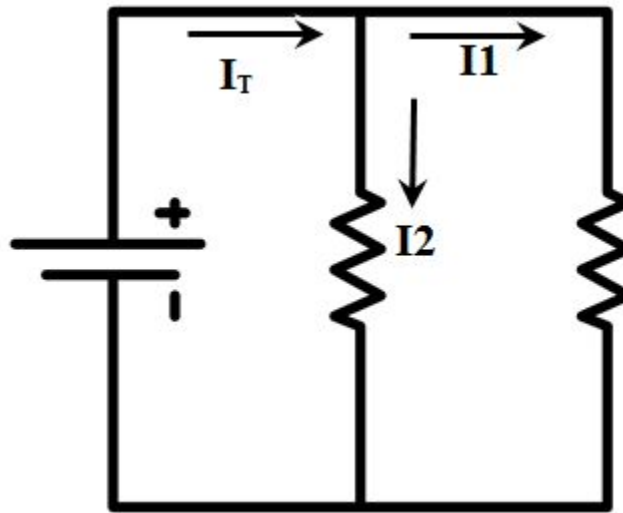

- Total current is the sum of the individual currents

$$I_T = I_1 + I_2 + \dots$$

# Parallel Circuits (2)

$$\begin{aligned} R_T &= \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots} \\ &= \frac{R_1 \times R_2}{R_1 + R_2} \text{ (if 2 only)} \\ &= \frac{R}{n} \text{ (if the same value)} \end{aligned}$$



# Diodes

- They allow electricity to flow through them in a certain direction only.
- Used in almost all types of electronics.
- Look like resistors but they do not have coloured stripes on them.



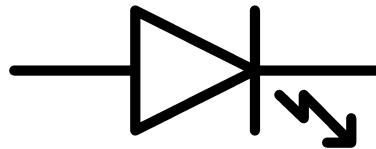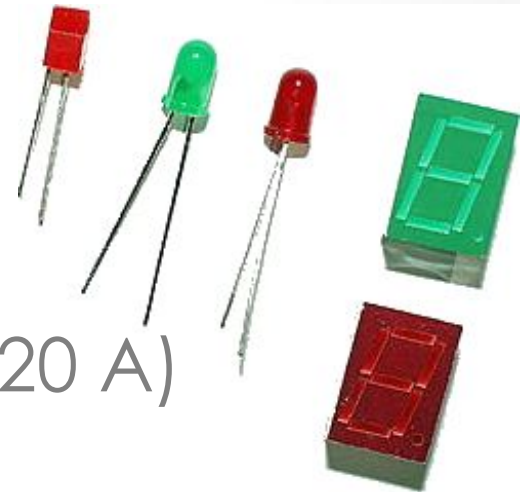
# Light Emitting Diodes

- A type of diode designed to emit light
- Can be visible or IR
- 2 V voltage drop
- Typically draws 20 mA (0.020 A)
- Schematic Symbol...



# A Simple LED Circuit

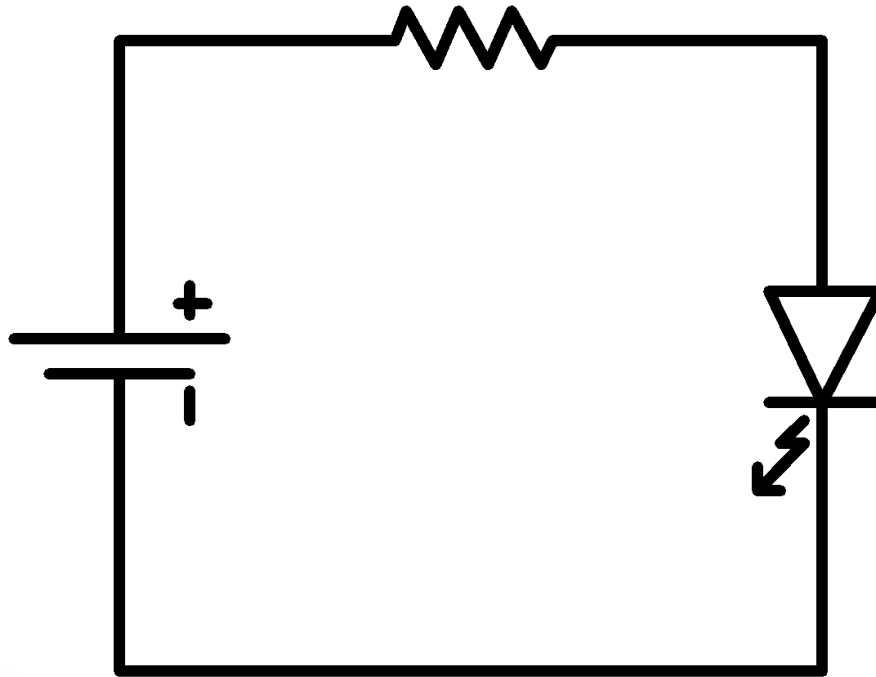


# Analyzing a LED Circuit with KVL and Ohm's Law

$$V_T = V_R + V_{LED}$$

$$I_{LED} = I_R = 20\text{ mA}$$

$$\begin{aligned} V_R &= V_T - V_{LED} \\ &= 9 - 2 \\ &= 7\text{ V} \end{aligned}$$
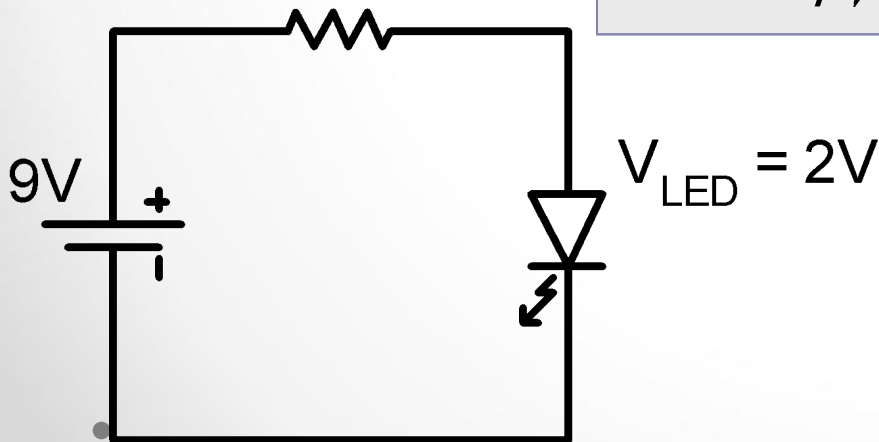
$$\begin{aligned} R &= \frac{V_R}{I_R} \\ &= \frac{7\text{ V}}{0.020\text{ A}} \\ &= 350\ \Omega \end{aligned}$$





# More about LEDs:

- <http://www.thebox.myzen.co.uk/Tutorial/LEDs.html>


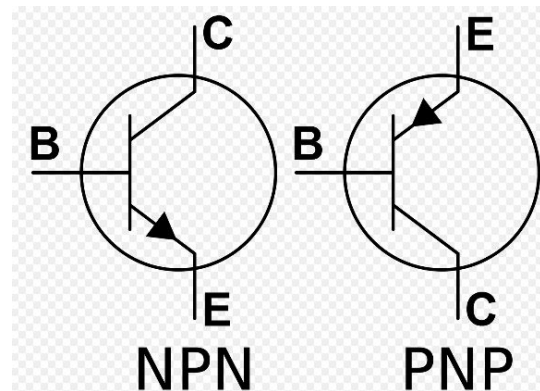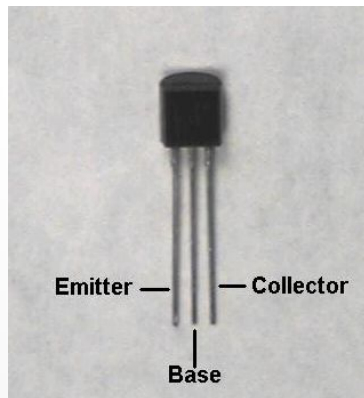
# Transistors

- They are used to amplify weak signals
- Also used as switches to (dis)connect other components.
- There are PNP and NPN types
- They have 3 connection points B (base) C (collector) and E (emitter).



# Capacitors

- They store electrical energy to smooth out the flow of AC current.
- They also block DC (Direct Current) and allow the flow of AC (Alternating Current) through a circuit
- The farad is the measure of the capacitance (electrical storage capacity)
- A farad is extremely large so many of the values measured are in microfarads.

