

# What is a 555 Timer?

---

- The 555 timer is an 8-pin IC that is capable of producing accurate time delays and/or oscillators.
- In the time delay mode, the delay is controlled by one external resistor and capacitor.
- In the oscillator mode, the frequency of oscillation and duty cycle are both controlled with two external resistors and one capacitor.



# What is a 555 Timer?

---


## Applications:

- basic timing functions: turning a light on for a certain amount of time
- create a warning light that flashes on and off
- create musical notes of a certain frequency
- control the positioning of a servo motor



# Pin Layout

---

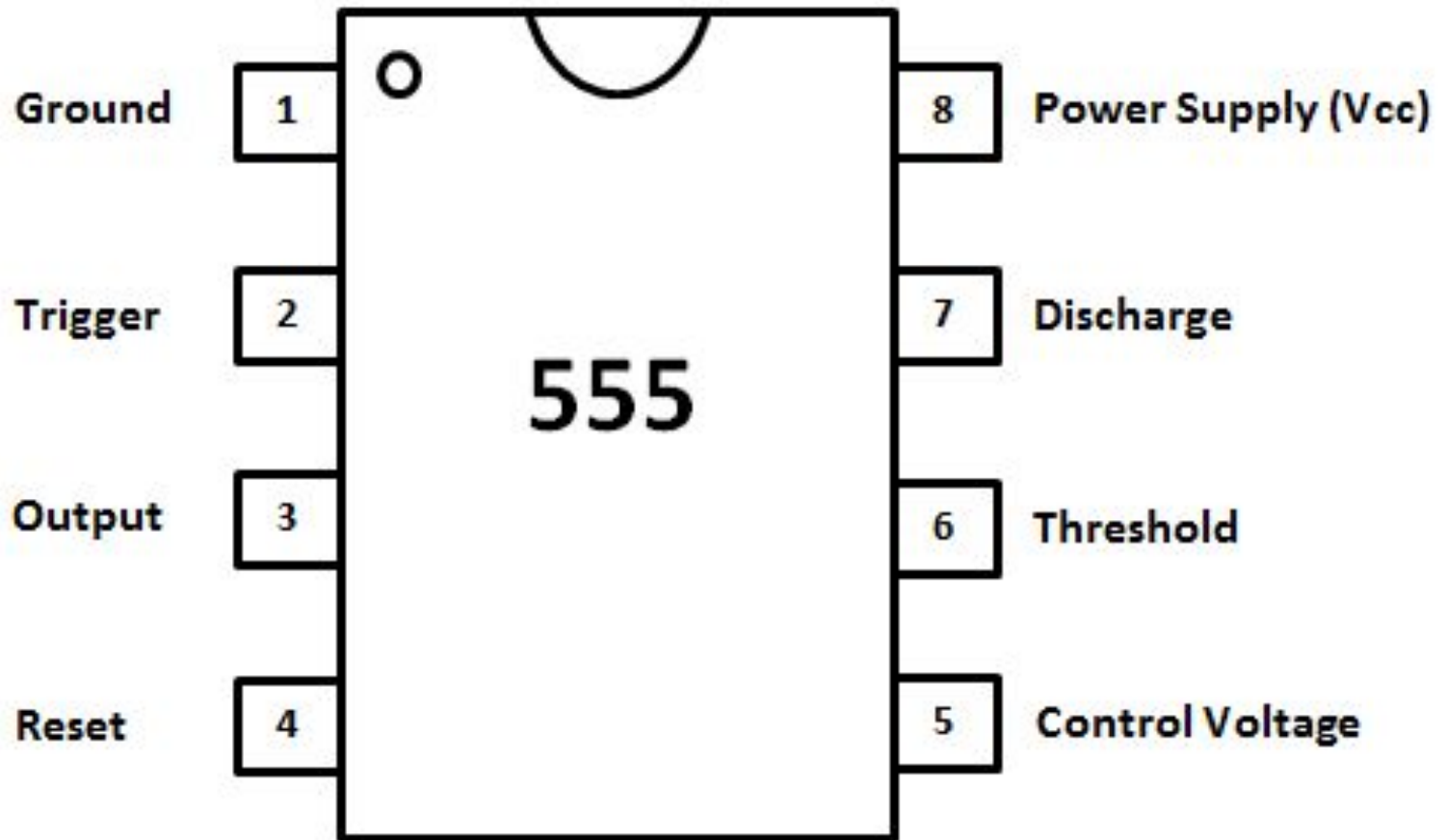

# Pin Explanations

---

- **Ground:** Pin 1 is connected to ground (-)
- **VCC:** Pin 8 is connected to the positive supply voltage.  $15\text{ V} \Rightarrow V_{cc} \geq 4.5\text{ V}$
- **Output:** Pin 3 is the output pin. The output is either low, which is very close to 0 V, or high, which is close to the supply voltage that's placed on pin 8.

# Pin Explanations

---

- **Output:** The exact shape of the output — that is, how long it's high and how long it's low, depends on the connections to the remaining five pins:
  - a. Trigger
  - b. Discharge
  - c. Threshold
  - d. Control
  - e. Reset

# 555 Timer Overview

element14  
presents


## HOW 555 TIMERS WORK

**PIN 8** (+Vcc)  
**PIN 5** (Control Voltage)  
**PIN 6** (Threshold)  
**PIN 4** (Power)  
**PIN 7** (Discharge)  
**PIN 1** (GND)  
**PIN 2** (Trigger)  
**PIN 3** (Output)


INSPIRE THE FUTURE  
THE LEARNING CIRCUIT 62

# 555 Timer Modes

element14  
presents **555 TIMER MODES EXPLAINED**



**THE LEARNING CIRCUIT** **66**

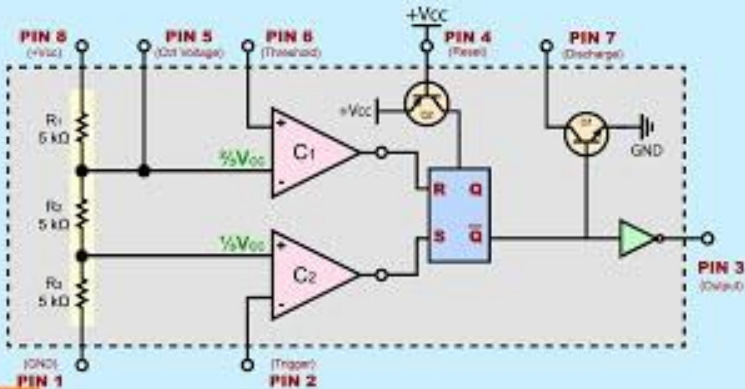

# Pin Explanations

---

**Trigger (2)** - Make the output high when input is  $< \frac{1}{3} V_{cc}$  (Active LOW)

**Reset (4)**- Resets circuit when voltage  $< 0.8V$  (Active LOW)


**Discharge (7)** - This pin is used to discharge an external capacitor that works in conjunction with a resistor to control the timing interval.

**Threshold (6)** - The purpose of this pin is to monitor the voltage across the capacitor that's discharged by pin 7. When this voltage reaches two thirds of the supply voltage ( $V_{cc}$ ), the timing cycle ends, and the output on pin 3 goes low.


**Control (5)** - Voltage applied with varying the timing frequency of the output. Usually connected to ground through a small capacitor. The purpose of the capacitor is to level out any fluctuations in the supply voltage that might affect the operation of the timer.



# Block Diagram for a 555 Timer

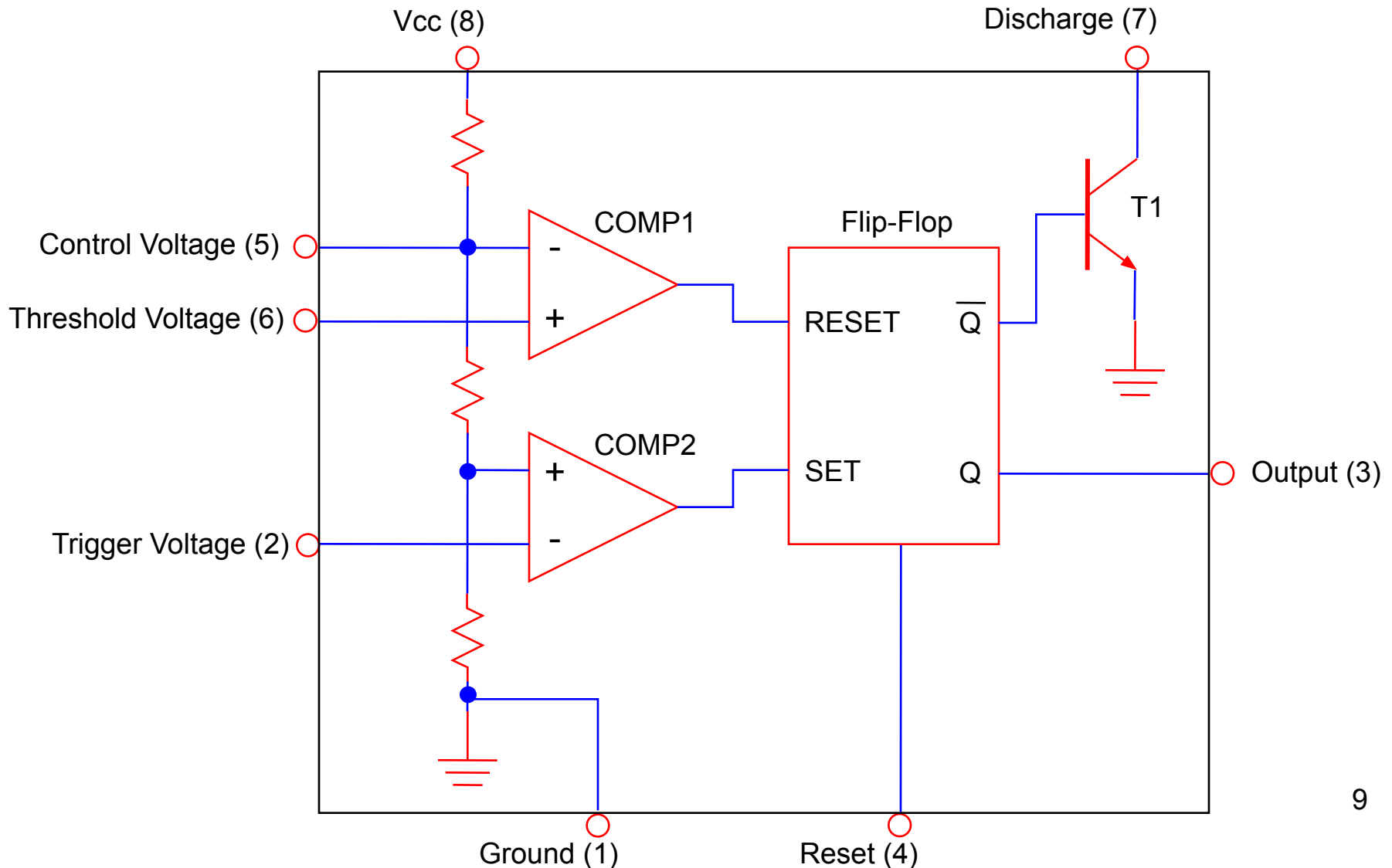
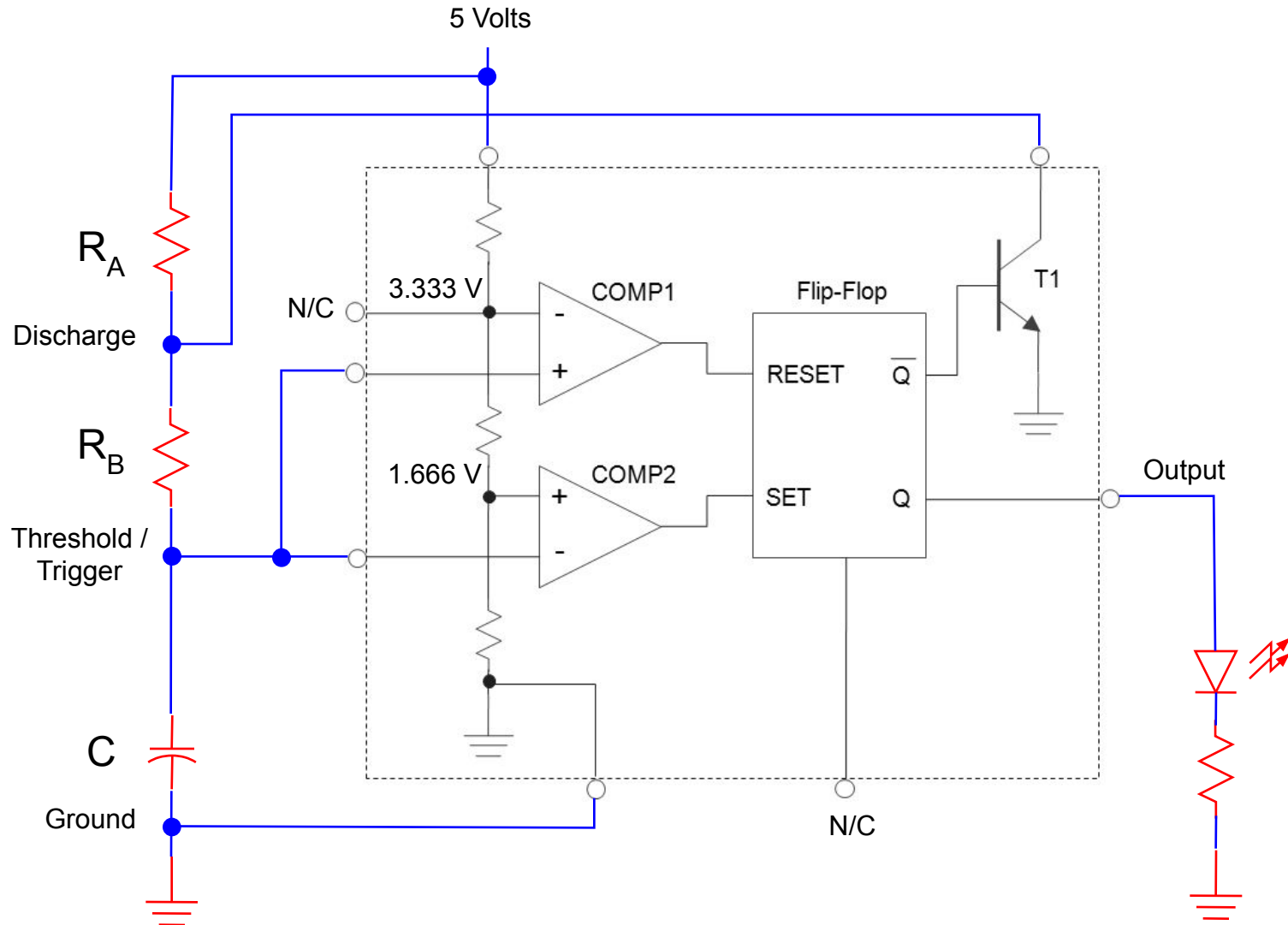
# Schematic of a 555 Timer in Oscillator Mode



# 555 Timer – Period / Frequency / DC

Period:

$$t_{\text{HIGH}} = 0.693 (R_A + R_B) C$$

$$t_{\text{LOW}} = 0.693 R_B C$$

$$T = t_{\text{HIGH}} + t_{\text{LOW}}$$

$$T = [0.693 (R_A + R_B) C] + [0.693 R_B C]$$

$$T = 0.693 (R_A + 2R_B) C$$

Duty Cycle:

$$DC = \frac{t_{\text{HIGH}}}{T} \times 100\%$$

$$DC = \frac{0.693 (R_A + R_B) C}{0.693 (R_A + 2R_B) C} \times 100\%$$

$$DC = \frac{(R_A + R_B)}{(R_A + 2R_B)} \times 100\%$$

Frequency:


$$F = \frac{1}{T}$$

$$F = \frac{1}{0.693 (R_A + 2R_B) C}$$

# Example: 555 Oscillator

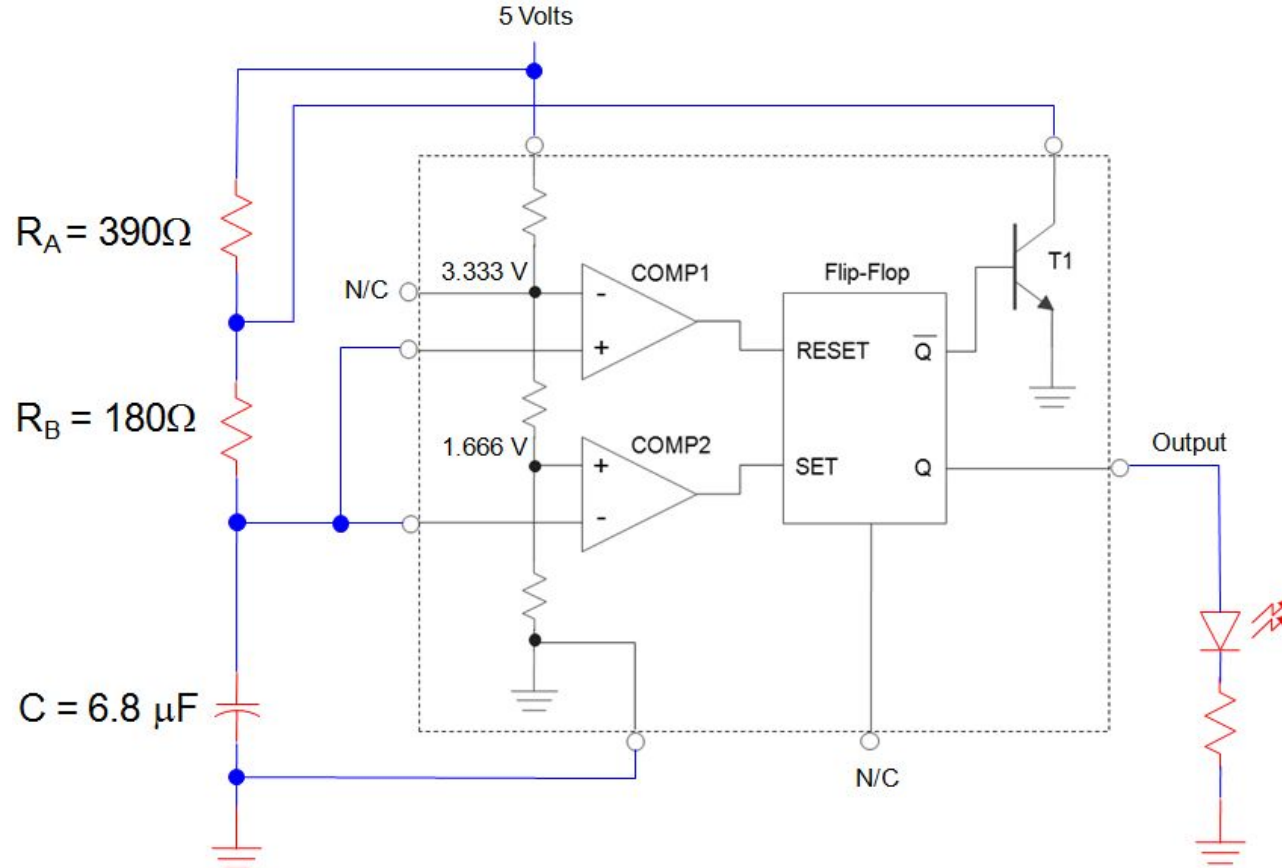*Example:*

For the 555 Timer oscillator shown below, calculate the circuit's, period (T), frequency (F), and duty cycle (DC).



# Example: 555 Oscillator

*Solution:*

$$R_A = 390 \, \Omega \quad R_B = 180 \, \Omega \quad C = 6.8 \, \mu\text{F}$$

Period:

$$T = 0.693 (R_A + 2R_B) C$$

$$T = 0.693 (390 \, \Omega + 2 \times 180 \, \Omega) \times 6.8 \, \mu\text{F}$$

$$T = 3.534 \, \text{mSec}$$

Frequency:

$$F = \frac{1}{T}$$

$$F = \frac{1}{3.534 \, \text{mSec}}$$

$$F = 282.941 \, \text{Hz}$$

Duty Cycle:

$$\text{DC} = \frac{(R_A + R_B)}{(R_A + 2R_B)} \times 100\%$$


$$\text{DC} = \frac{(390 \, \Omega + 180 \, \Omega)}{(390 \, \Omega + 2 \times 180 \, \Omega)} \times 100\%$$

$$\text{DC} = 76\%$$

# Example: 555 Oscillator

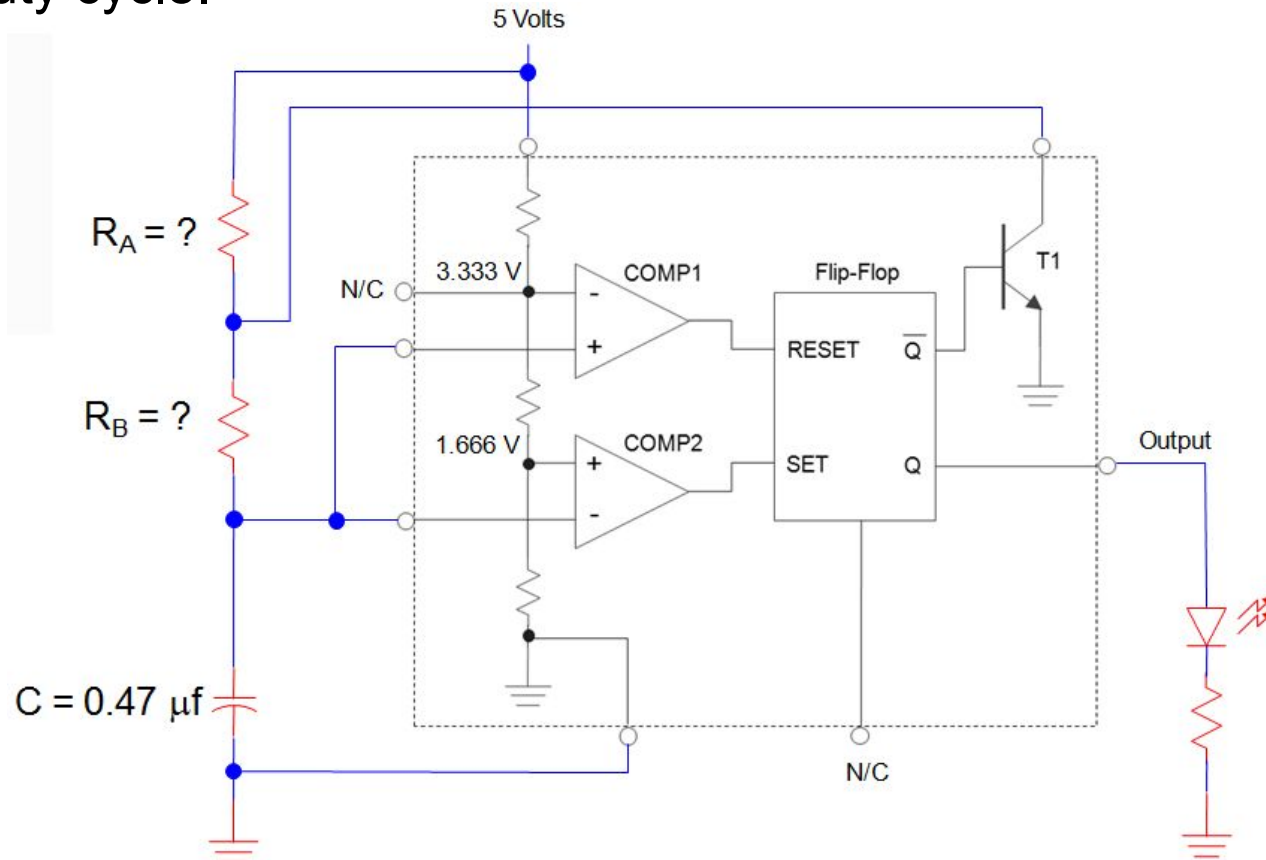*Example:*

For the 555 Timer oscillator shown below, calculate the value for  $R_A$  &  $R_B$  so that the oscillator has a frequency of 2.5 KHz @ 60% duty cycle.



# Example: 555 Oscillator

*Solution:*

Frequency:

$$T = \frac{1}{f} = \frac{1}{2.5 \text{ kHz}} = 400 \mu\text{Sec}$$

$$T = 0.693 (R_A + 2R_B) C = 400 \mu\text{Sec}$$

$$T = 0.693 (R_A + 2R_B) 0.47 \mu\text{f} = 400 \mu\text{Sec}$$

$$R_A + 2R_B = \frac{400 \mu\text{Sec}}{0.693 \times 0.47 \mu\text{f}} = 1228.09 \Omega$$

$$R_A + 2R_B = 1228.09$$

Duty Cycle:

$$\text{DC} = \frac{(R_A + R_B)}{(R_A + 2R_B)} \times 100\% = 60\%$$

$$\frac{(R_A + R_B)}{(R_A + 2R_B)} = 0.6$$

$$R_A + R_B = 0.6(R_A + 2R_B)$$

$$R_A + R_B = 0.6 \times R_A + 1.2 \times R_B$$

$$0.4 \times R_A = 0.2 \times R_B$$

$$R_A = 0.5 \times R_B$$

Two Equations & Two Unknowns!

# Example: 555 Oscillator

*Solution:*

Frequency:

$$R_A + 2R_B = 1228.09$$

Duty Cycle:

$$R_A = 0.5 \times R_B$$

Substitute and Solve for  $R_B$

$$R_A + 2R_B = 1228.09 \Omega$$

$$0.5 \times R_B + 2R_B = 1228.09 \Omega$$

$$2.5R_B = 1228.09 \Omega$$

$$R_B = 491.23 \Omega$$

Substitute and Solve for  $R_A$

$$R_A + 2R_B = 1228.09 \Omega$$

$$R_A + 2(491.23 \Omega) = 1228.09 \Omega$$

$$R_A + 982.472 \Omega = 1228.09 \Omega$$

$$R_A = 245.618 \Omega$$