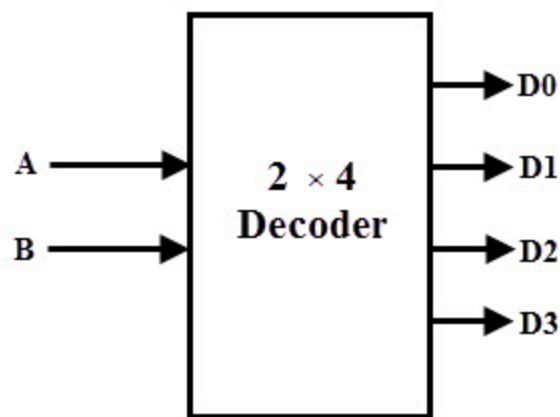


2:4 Binary Decoder Exercise



Summary:

The inputs B and A represent a binary sequence.
B represents the 2’s column
A represents the 1’s column

When the inputs (BA) representing a binary sequence evaluates to 0, only D0 turns on.
When the inputs (BA) representing a binary sequence evaluates to 1, only D1 turns on.
Etc ...

Fill out the chart.

B (2 ¹ column)	A (2 ⁰ column)	D0	D1	D2	D3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1


What are the equations for each output LED (D0 to D3)?

- D0: $\overline{A} \bullet \overline{B}$
- D1: $A \bullet \overline{B}$
- D2: $\overline{A} \bullet B$
- D3: $A \bullet B$


Open up Logisim and wire the circuit for each output. Take a screenshot of your circuit for each combination of A and B that produces a different output.

Scenario 1: (Explain briefly here)

2:4 Binary Decoder Exercise

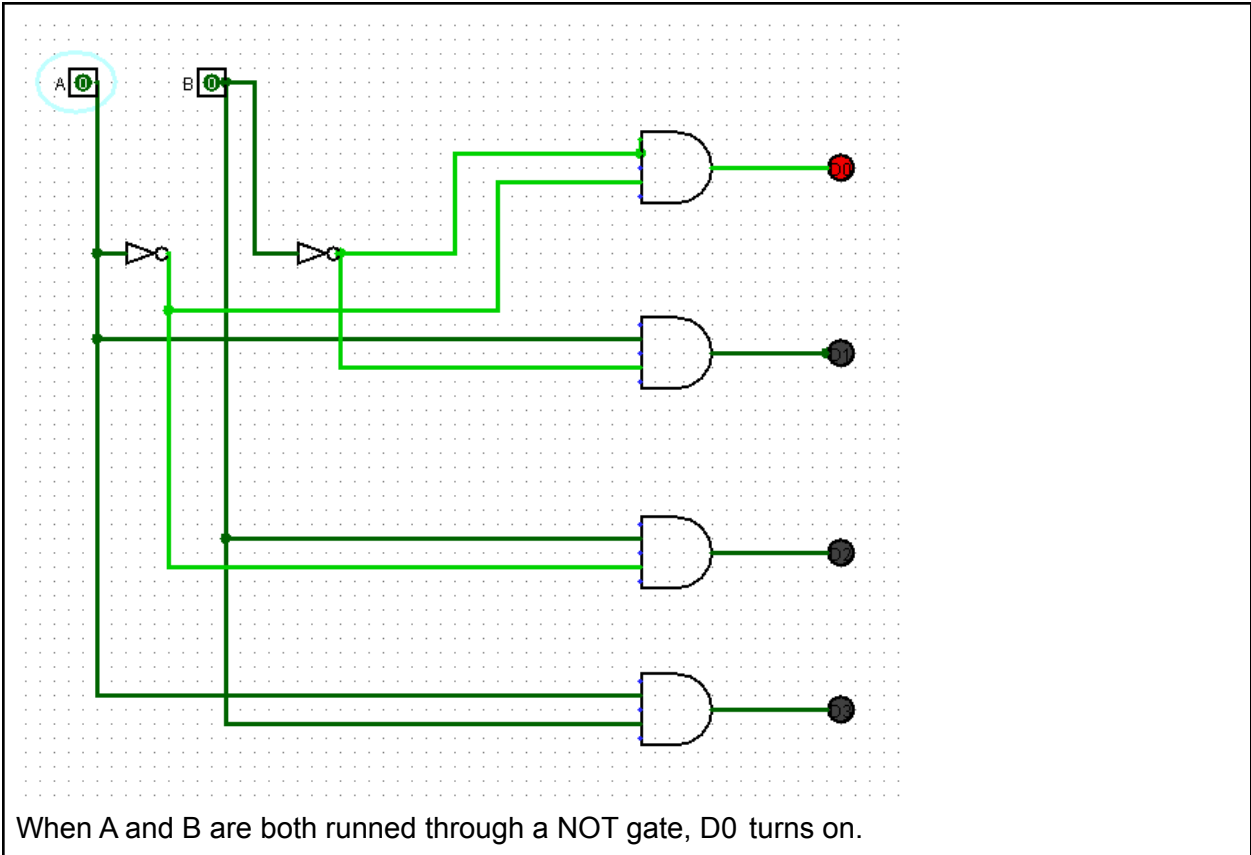


Scenario 2: (Explain briefly here)

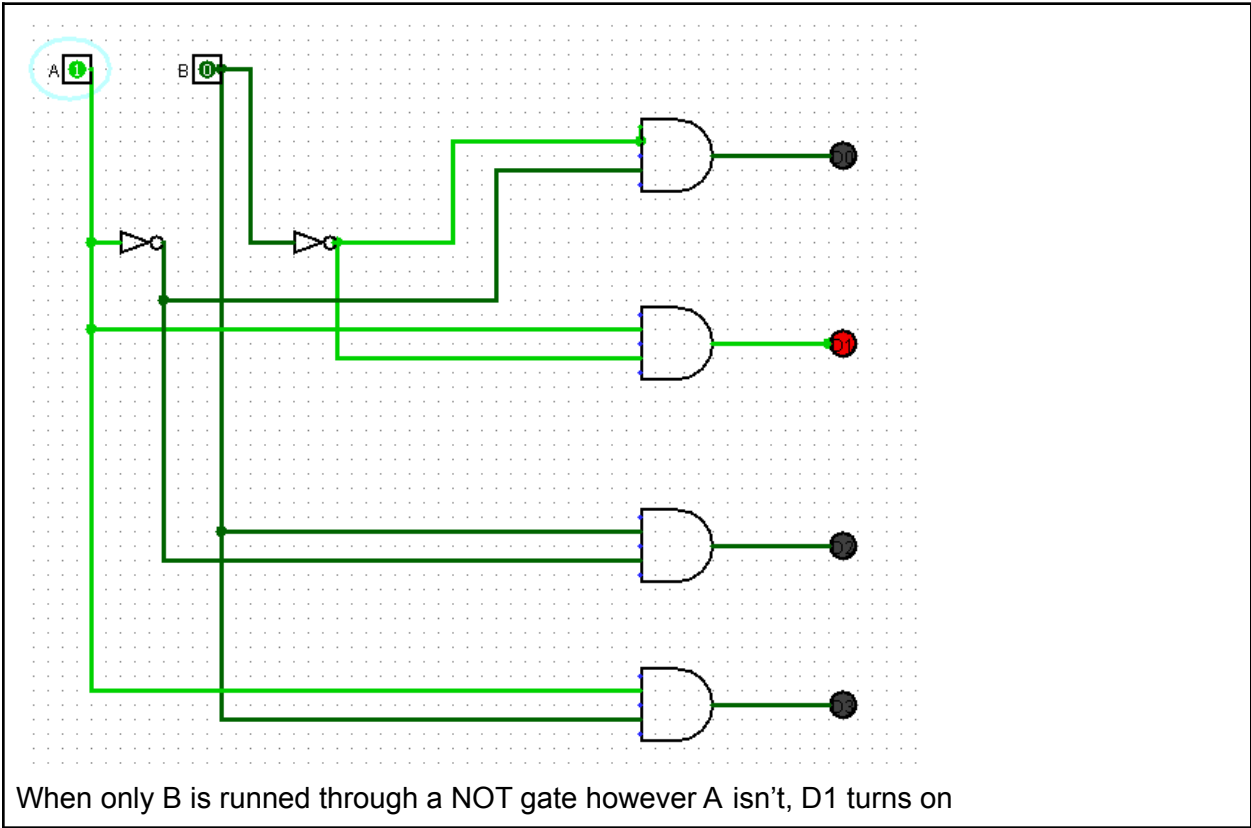

Scenario 3: (Explain briefly here)

2:4 Binary Decoder Exercise

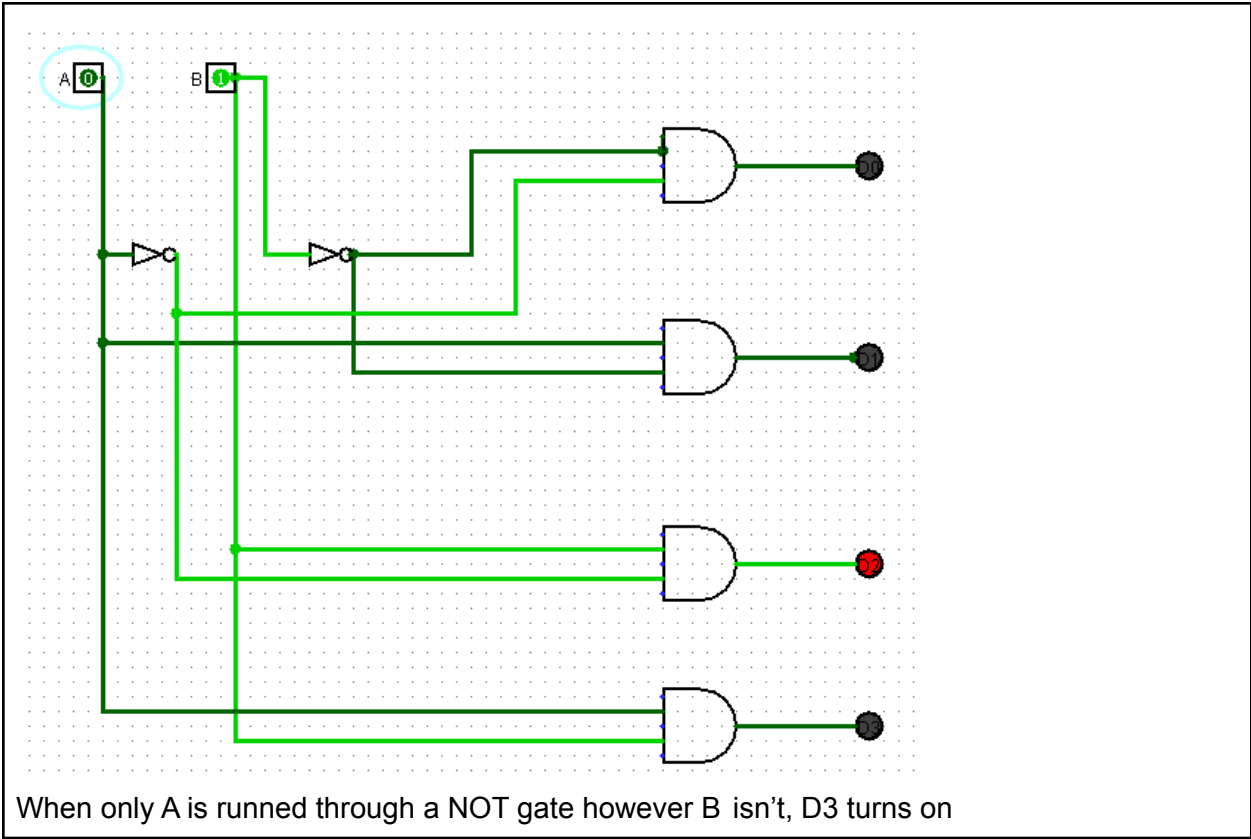

Scenario 4: (Explain briefly here)

